



B.Sc. PHYSICS – I YEAR
DJK1B : BASIC ELECTRONICS
SYLLABUS

Unit I : Diodes

P-n junction diode – characteristics – Regulation with zener diodes – Bridge rectifier – clipping and clamping circuits with diodes.

Unit II : Transistors and Amplifiers

Transistors – Transistor action – three modes of connection – biasing – load line and Q –point – voltage divider bias – stabilization – CE amplifier.

Unit III : Oscillators

Principles of negative voltage feed back in amplifiers – gain – advantages – principle of negative current feedback – Oscillation – Bark Hausen criterion for oscillation – colpitt's oscillator

Unit IV : Field Effect Transistor

Principle , features and characteristics of FET – JFET and MOSFET – their characteristics – enhancement and depletion type

Unit V : Operational Amplifier

Characteristics – slew rate – inverting and non-inverting amplifier – adder – sub tractor – integrator – differentiator

Books for study and reference:

1. Fundamentals of Electronics – B. Ghosh
2. Principles of Electronics - V.K. Mehtha



UNIT I : DIODES

P-N junction diode – characteristics – Regulation with zener diodes – Bridge rectifier – clipping and clamping circuits with diodes.

1.1 Semiconductors

Semiconductor is a solid substance that has a conductivity between that of an insulator and that of metal due to the addition of an impurity. Devices made of semiconductors, are the essential components of most electronic circuits. Semiconductors include antimony, arsenic, boron, carbon, germanium, selenium, silicon, sulfur, and tellurium. Silicon is the best-known of these, forming the basis of most integrated circuits . Common semiconductor compounds include gallium arsenide, indium antimonide, and the oxides of most metals. Of these, gallium arsenide (Ga-As) is widely used in low-noise, high-gain, weak-signal amplifying devices.

Types of Semiconductors: Semiconductors are mainly classified into two categories: They are (a) Intrinsic Semiconductors and (b) Extrinsic Semiconductors

(a) Intrinsic Semiconductor

An electron is called a negative charge carrier and a hole (absence of an electron) is called a positive charge carrier. An intrinsic semiconductor material is chemically very pure and possesses poor conductivity. It has equal numbers of negative charge carriers and positive charge carriers. A silicon crystal is different from an insulator because at any temperature above absolute zero, there is a finite probability that an electron in the lattice will be knocked loose from its position, leaving behind an electron deficiency or a *hole*.

If a voltage is applied, then both the electron and the hole can contribute to a small current flow. The conductivity of a semiconductor can be modelled in terms of the band theory of solids. The band model of a semiconductor suggests that at ordinary temperatures there is a finite probability that electrons can reach the conduction band and contribute to electrical conduction.



(b) Extrinsic Semiconductor

An extrinsic semiconductor is an improved intrinsic semiconductor with a small amount of impurities added by a process, known as *doping*. This alters the electrical properties of the semiconductor and improves its conductivity. Introducing impurities into the semiconductor materials can control their conductivity. Doping process produces two groups of semiconductors: the majority negative charge conductor (n-type) and the positive charge conductor (p-type). Semiconductors are available as either elements or compounds. Silicon and Germanium are the most common elemental semiconductors.

1.2 Doping of Semiconductors

Pentavalent impurities (5-valence electrons) produce n-type semiconductors by contributing extra electrons. Trivalent impurities (3-valence electrons) produce p-type semiconductors by producing a hole or electron deficiency.

(a) n-Type Semiconductor

The addition of pentavalent impurities [fig. 1.1] such as antimony, arsenic or phosphorous contributes free electrons, greatly increasing the conductivity of the intrinsic semiconductor. In this type, the current conduction is mainly due to the electrons, and the holes are the minority carriers. This forms n-type semiconductor.

 


Fig. 1.1

 


Fig. 1.2




(b) p-Type Semiconductor

The addition of trivalent impurities [fig. 1.2] such as boron, aluminum or gallium to an intrinsic semiconductor creates deficiencies of valence electrons, called *holes*. In this type, the current conduction is mainly due to the holes, and the electrons are the minority carriers. This forms p-type semiconductor.

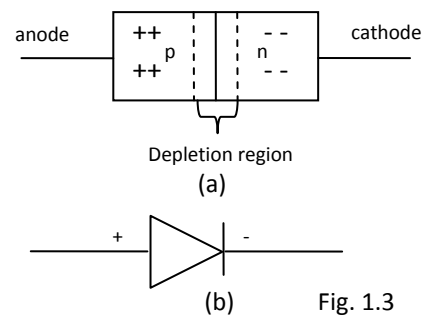1.3 p-n Junction Diode

When n-doped and p-doped semiconductor are fused together to form a junction, electrons migrate from the n-side into the p-side and holes migrate from the p-side into the n-side. Following this transfer, the diffused electrons come into contact with holes on the p-side and are eliminated by recombination. Likewise for the diffused holes on the n-side. The net result is a region with no mobile carriers. This region is called *depletion region*. The symbols used for a p-n junction diode are shown in the fig. 1.3



1.4 Energy Band Diagram of p-n junction diode

The *Fermi energy* is defined as the energy difference between the highest and lowest occupied single-particle states in a quantum system of non-interacting fermions at absolute zero temperature. For n-type semiconductor, the Fermi level E_F lies near the conduction band edge E_C but for p-type semiconductor, E_F lies near the valence band edge E_V . Now,

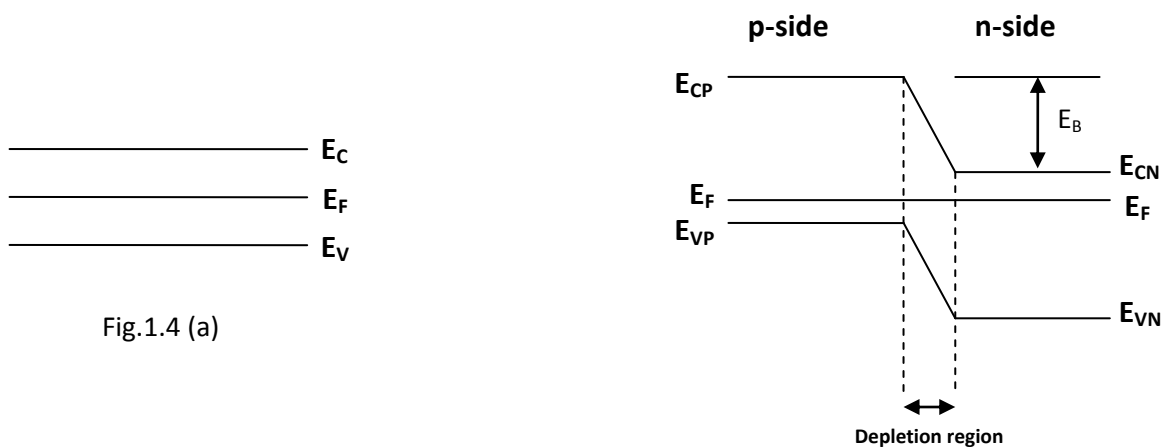


Fig.1.4 (a)

Fig.1.4 (b)



when a p-n junction is built, the Fermi energy E_F attains a constant value [fig. 1.4(b)]. In this situation the p-side conduction band edge. Similarly n-side valance band edge will be at higher level than E_{cn} , n-sides conduction band edge of p - side. This energy difference is known as barrier energy. The barrier energy is $E_B = E_{cp} - E_{cn} = E_{vp} - E_{vn}$ If we apply reverse bias

 


Fig.1.4 (c)


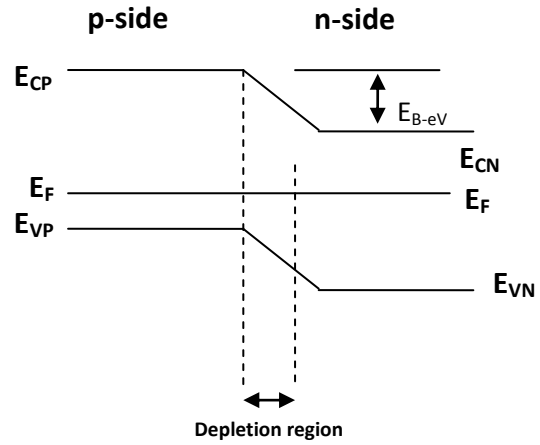


Fig.1.4 (d)

voltage V , across the junction, then the barrier energy increases by an amount of eV (fig. 1.4(c)) and if is forward bias is applied, the barrier energy decreases by eV [fig. 1.4(d)]

 1.5 Forward and reverse biased p-n Junction

Biasing means application of voltage. To make a p-n junction to conduct, electrons should move from the n-type region to the p-type region and holes moving in the reverse direction. To overcome the potential barrier across the junction, a battery is connected to the two ends of the p-n junction diode. The battery can be connected to the p-n junction in two ways:



Forward bias

Reverse bias

(a)

(b)

Fig. 1.5

○ holes
● electrons



Positive terminal of the battery connected to the p-side and negative terminal of the battery connected to the n-side. This is called *forward bias* [fig. 1.5(a)]. If positive terminal of the battery is connected to the n-side and negative terminal of the battery connected to the p-side, then it is called *reverse bias* [fig. 1.5(b)].

When a junction is forward biased and the bias exceeds barrier potential, holes are compelled to move towards the junction and cross from the p-region to the n-region. Similarly, electrons cross the junction into the p-region. This sets in forward current in the diode. The current increases with voltage and is of the order of a few milli-amperes. Under the forward bias condition, the junction offers low resistance to flow of current. The value of junction resistance, called forward resistance, is in the range 10Ω to 30Ω .

When the p-n junction is reverse biased, holes in the p-region and electrons in the n-region move away from the junction. A small current flows even now. This small current caused by minority carriers is called reverse saturation current or leakage current. Thus a p-n junction offers a low resistance when forward biased, and high resistance when reverse biased. This property of p-n junction is used for ac to dc rectification. When the reverse bias voltage is of the order of a few hundred volt, the current through the p-n junction increases rapidly and damages it due to excessive power dissipation. The voltage at which a diode breaks down is termed as *breakdown voltage*. When a reverse bias is applied, a large electric field is established across the junction. This field will:

- (i) accelerate the available minority carriers, which in turn, collide with the atoms of the semiconductor material and eject more electrons through energy transfer (*avalanche effect*)
- (ii) break covalent bonds by exerting large force on electrons bound by the bonds. This results in creation of additional electron-hole pairs in the junction region .

1.6 Characteristics study of a junction diode

(i) Forward bias characteristics

Circuit Connections are made as shown in the fig. 1.6(a) using a p-n junction diode. Initially the voltage applied to the diode is varied in steps of 0.1 V by using the rheostat (R_h). Once the current starts increasing, the voltage is varied from 1V to 12V in steps of 1V and the



corresponding forward biased voltage readings (V_f) in the voltmeter (V) and the corresponding forward biased current (I_f) in the milli ammeter (mA) are noted and the readings are tabulated as shown in the table. A suitable graph is drawn by taking V_f on x-axis and I_f on y-axis. This gives the forward bias characteristic curve.

 


Fig. 1.6(a)

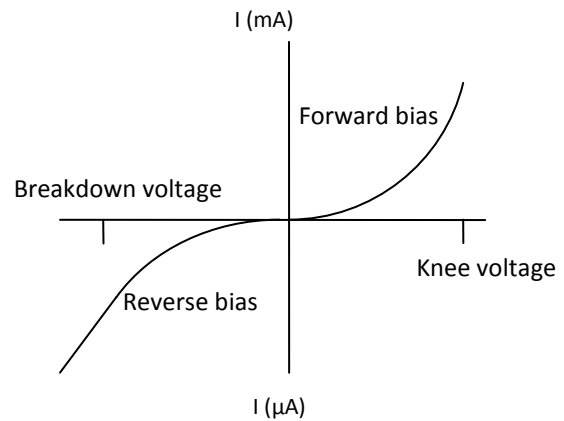


Fig. 1.6(b)

(ii) Reverse bias characteristics

To study the reverse bias characteristics of the diode, a circuit connection is made as shown in the fig. 1.6(a), but with the polarities of the diode are changed and the milliammeter is replaced with a micro ammeter. The procedure is repeated as in forward bias mode and the readings are tabulated. A suitable graph is drawn giving the reverse bias characteristic curve for the given p-n diode.

S.No.	Forward / Reverse bias in volts	Forward bias/Reverse bias current in mA/ μ A

TABLE 1

The characteristic curve for a p-n junction diode is shown in the fig.1.6 (b). In the forward bias mode, the current increases very slowly in the beginning and then increases rapidly.



The point at which the current starts to increase rapidly is known as knee voltage. In the reverse mode, the current increases with voltage and reaches a point where it remains almost constant with further increase in voltage. This voltage is called *break down voltage* of the given diode.

1.7 Zener Diode

A Zener Diode is a special kind of diode which permits current to flow in the forward direction as normal, but will also allow it to flow in the reverse direction when the voltage is above a certain value, the breakdown voltage known as the Zener voltage. The symbol used is shown in the fig. 1.7(a)

 


Fig. 1.7 (a)

 


Fig. 1.7 (b)

The zener voltage of a standard diode is high, but if a reverse current above that value is allowed to pass through it, the diode is permanently damaged. Zener diodes are designed so that, when a reverse current above the zener voltage passes through a zener diode, there is a controlled breakdown which does not damage the diode. The voltage drop across the zener diode is equal to the zener voltage of that diode. The fig. 1.7 (b) shows a current vs. voltage graph. With a zener diode connected in the forward direction, it behaves exactly the same as a standard diode. In the reverse direction however there is a very small *leakage current* between 0V and the zener break down voltage. Then, when the voltage reaches the breakdown voltage (V_z), suddenly current flows freely through it.



Uses of Zener Diodes

- 1) They are used as reference voltages for circuits.
- 2) Zener diodes are used to regulate the voltage in electric circuits.
- 3) They are used as over voltage protector.

1.8 Zener Diode as Voltage Regulator

A voltage regulator circuit can be designed using a zener diode to maintain a constant DC output voltage across the load in spite of variations in the input voltage or changes in the load current. The zener diode is always operated in its reverse biased condition.

 


Fig. 1.8

In the fig. (1.8), by using Kirchoff's current law, we can write

$$I_s = I_z + I_L$$

If I_L decreases due to change in load resistance, I_z increases since I_s is constant. Even then V_z remains constant. When I_L increases, I_z decreases to keep I_s constant. Thus V_z is always constant. That is the voltage across the load is always constant.

Also, when V_s exceeds the rated voltage of the device, the breakdown voltage is reached at which avalanche breakdown occurs in the semiconductor depletion layer of the zener diode and a current starts to flow through the diode, thus maintaining a constant current flow




through the load. The current now flowing through the zener diode increases dramatically to the maximum circuit value, which is usually limited by a series resistor and once achieved this reverse saturation current remains constant over a wide range of applied voltages. The voltage point at which the voltage across the zener diode becomes stable is called the *zener voltage*. For zener diodes this voltage can range from less than one volt to hundreds of volts.

 1.9 Bridge Rectifier

Construction

A Bridge rectifier is an alternating current (AC) to direct current (DC) converter. The bridge rectifier circuit diagram is shown in the fig. 1.9. It consists of a step down transformer which converts the AC mains 230V to 12V AC supply. Next stage uses four diodes in the form of a bridge as shown. Since the output after the diode bridge rectifiers is of pulsating, a filter circuit is used. The filter consists of one or more capacitors across the load.



Working

During the positive half cycle of secondary voltage, diodes D2 and D3 are forward biased and diodes D1 and D4 are reverse biased. Now the current flows through D2, Load (R_L) and D3. During the negative half cycle of the secondary voltage, diodes D1 and D4 are forward biased and rectifier diodes D2 and D3 are reverse biased. Now the current flows



through D4, Load and D1. In both the cycles, load current flows in the same direction. Hence we get a pulsating DC voltage as shown in fig 1.10. So a filter circuit is added to reduce the pulsation in the output wave form.

1.10 Capacitor filter

A capacitor is shunted across the output of a rectifier. This capacitor is also shunted with a load resistor. This addition of a capacitor at the output converts the pulsating DC voltage to fixed DC voltage. Upto a time period (say $t=1s$) input voltage is increasing, so the capacitor charges up to a peak value of the input. After $t=1s$, the input starts to decrease, then the voltage across the capacitor reverse biases the diodes D2 and D4 and therefore these diodes will not conduct. Now capacitor discharges through the load and hence voltage across the capacitor decreases. When the peak voltage exceeds the capacitor voltage, diodes D2 or D4 are forward biased and as a result capacitor again charges to the peak value. This process continues. Hence we get almost smooth DC voltage as shown in fig. (1.11).

 


Fig. 1.11

1.11 Ripple factor

Small unwanted residual periodic variation of the direct current (DC) output of a power supply which has been derived from an alternating current (AC) source is called *ripple*. Ripple factor (γ) is defined as the ratio of the root mean square (rms) value of the ripple voltage to the absolute value of the DC component of the output voltage. It is expressed as a percentage.

1.12 Effects of ripple

Ripple is undesirable in many electronic applications for a variety of reasons. They are,



- 1) The ripple frequency and its harmonics are within the audio band and will therefore be audible on equipment such as radio receivers, equipment for playing recordings and professional studio equipment.
- 2) The ripple frequency is within television video bandwidth. Analogue TV receivers will exhibit a pattern of moving wavy lines if too much ripple is present.
- 3) The presence of ripple can reduce the resolution of electronic test and measurement instruments. In an oscilloscope, it will manifest itself as a visible pattern on screen.
- 4) Within digital circuits, it reduces the threshold, at which logic circuits give incorrect outputs and data is corrupted.
- 5) High-amplitude ripple currents shorten the life of electrolytic capacitors.

1.13 Peak Inverse Voltage (PIV)

Peak Inverse Voltage or Peak Reverse Voltage (PRV) refers to the maximum voltage a diode or other device can withstand in the reverse-biased direction before it breaks down. In a rectifier circuit, during negative half cycle, the diode is reverse biased and the whole input voltage appears across the diode. When the input reaches its peak value V_m , in the negative half cycle, the voltage across the diode is maximum. This is the PIV of the given diode. In rectifier design two important parameters must be considered.

1. The current handling capacity required of the diode
2. Peak Inverse Voltage that the diode must withstand without breakdown. It is desirable to select a diode having reverse breakdown voltage at least 50% more than that the expected PIV.

PROBLEM

The turn ratio of the transformer used in a bridge rectifier is 12:1. The primary is connected to 220V, 50 Hz power. Assuming the diodes to be ideal, find the dc voltage across the load. What is the PIV of each diode?

Given: $V_{rms} = 220 V$

Maximum primary voltage = $V_p = \sqrt{2} V_{rms} = 311 V$



If the maximum secondary voltage is V_s , then

$$\frac{V_p}{V_s} = \frac{12}{1} \quad (\text{since the turn ratio is 12:1})$$

$$\therefore V_s = V_p \frac{1}{12} = \frac{311}{12} = 25.9 \text{ volts}$$

$$\text{PIV} = V_s = 25.9 \text{ V}$$

$$\text{d.c. voltage across the load} = V_{dc} = \frac{2V_s}{\pi} = \frac{2 \times 25.9}{3.14} = 16.48 \text{ V}$$

PROBLEM

A power supply delivers 90 watts to a load of 1 kilo ohms. Find the a.c. voltage present across the load, if the ripple factor is 0.1%

Power delivered to the load

$$\begin{aligned} P &= \frac{V^2}{R} \quad \text{or} \quad V = \sqrt{PR} \\ &= \sqrt{90 \times 1000} = 300 \text{ V} \quad \text{since } P=90 \text{ and } R=1000 \\ \therefore V_{dc} &= 300 \text{ V} \end{aligned}$$

$$\text{Ripple factor } \gamma = \frac{V_{ac}}{V_{dc}} \quad \text{or} \quad V_{ac} = r \times V_{dc} = \frac{0.1}{100} \times 300 = 0.3 \text{ V}$$

1.14 Diode Clipping Circuits

The Diode Clipper, also known as a *Diode Limiter*, is a wave shaping circuit. It prevents the output of a circuit from exceeding a predetermined voltage level without distorting the remaining part of the applied waveform. It consists of resistors, junction diodes or transistors. Clipping is achieved either at one level or two levels.

(a) Positive Diode Clipping Circuits

In this diode clipping circuit fig. 1.12, the diode is forward biased during the positive half cycle of the sinusoidal input waveform. For the silicon diode to become forward biased, it



must have the input voltage magnitude greater than +0.7 volts (+0.3 volts for a germanium diode). When this happens the diode begins to conduct and holds the voltage across itself

 


Fig. 1.12

constant at 0.7V until the sinusoidal waveform falls below this value. Thus the output voltage which is taken across the diode can never exceed 0.7 volts during the positive half cycle. During the negative half cycle, the diode is reverse biased (cathode more positive than anode) blocking current flow through itself and as a result has no effect on the negative half of the sinusoidal voltage which passes to the load unaltered. Thus the diode limits the positive half of the input waveform and is known as a positive clipper circuit.

(b) Negative Diode Clipping Circuits

Here the reverse is true (fig. 1.13). The diode is forward biased during the negative half cycle of the sinusoidal waveform and limits or clips it to -0.7 volts while allowing the positive half cycle to pass unaltered when reverse biased. As the diode limits the negative half cycle of the input voltage it is called a negative clipper circuit.

 


Fig. 1.13



(c) Clipping of both half cycles

If we connect two diodes in inverse parallel as shown in fig. 1.14, then both the positive and negative half cycles would be clipped as diode D_1 clips the positive half cycle of

 


Fig. 1.14

the sinusoidal input waveform while diode D_2 clips the negative half cycle. Then diode clipping circuits can be used to clip the positive half cycle, the negative half cycle or both. For ideal diodes the output waveform above would be zero. However, due to the forward bias voltage drop across the diodes the actual clipping point occurs at $+0.7$ volts and -0.7 volts respectively. But we can increase this $\pm 0.7V$ threshold to any value we want up to the maximum value, (V_{PEAK}) of the sinusoidal waveform either by connecting together more diodes in series creating multiples of 0.7 volts, or by adding a voltage bias to the diodes.

1.15 Positive Biased Diode Clipping Circuits

To produce diode clipping circuits for voltage waveforms at different levels, a bias voltage, V_{Bias} is added in series with the diode as shown in fig. 1.15. The voltage across the series combination must be greater than $V_{Bias} + 0.7V$ before the diode becomes sufficiently forward biased to conduct. For example, if the V_{Bias} level is set at 4.0 volts, then the sinusoidal voltage at the diode's anode terminal must be greater than $4.0 + 0.7 = 4.7$ volts for it to become forward biased. Any anode voltage levels above this bias point are clipped off.

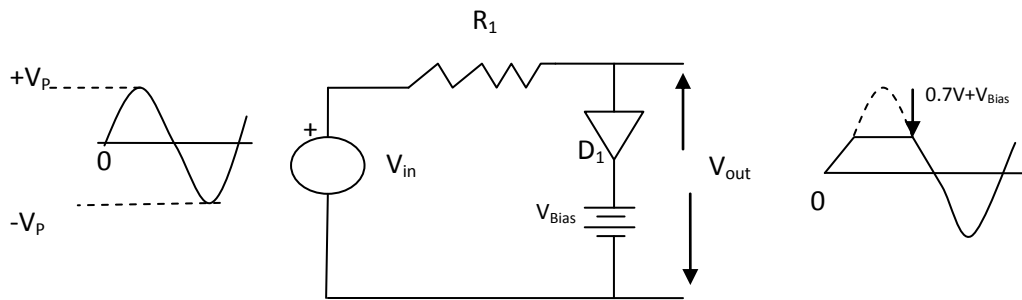


Fig. 1.15

(b) Negative Biased Diode Clipping circuits

Likewise, by reversing the diode and the battery bias voltage, when a diode conducts the negative half cycle of the output waveform is held to a level $-V_{BIAS} - 0.7V$ as shown in fig. 1.16

 


Fig. 1.16

(c) Biased Diode Clipping of both levels

If both the positive and the negative half cycles are to be clipped, then two biased clipping diodes are used. But for both positive and negative diode clipping, the bias voltage need not be the same. The positive bias voltage could be at one level, for example 4 volts, and the negative bias voltage at another, for example 6 volts as shown in fig. 1.17.

When the voltage of the positive half cycle reaches $+4.7 V$, diode D_1 conducts and limits the waveform at $+4.7 V$. Diode D_2 does not conduct until the voltage reaches $-6.7 V$. Therefore, all positive voltages above $+4.7 V$ and negative voltages below $-6.7 V$ are automatically clipped.

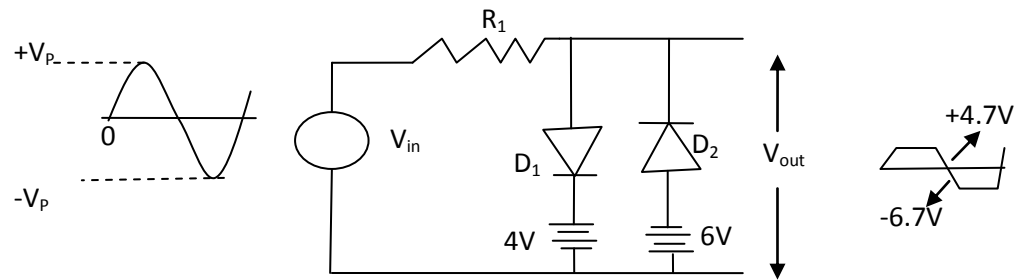


Fig. 1.17

The advantage of biased diode clipping circuits is that it prevents the output signal from exceeding preset voltage limits for both half cycles of the input waveform, which could be an input from a noisy sensor or the positive and negative supply rails of a power supply. If the diode clipping levels are set too low or the input waveform is too great then the elimination of both waveform peaks could end up with a square-wave shaped waveform.

Uses of Clipping circuits

1. They are used to change the shape of a waveform
2. They are used in Circuit transient protection
3. They are used in speech processing for communication
4. They are used to chop the overall signal down to size so that the excessive amplitude does not overload the subsequent stages and cause a malfunction
5. Diode clipping circuits can be used in voltage limiting applications.

1.16 Diode Clamping Circuits

Clampers can also be referred as DC restorers. Clamping circuits are designed to shift the input waveform either above or below the DC reference level without altering the shape of waveform. This shifting of the waveform results in a change in the DC average voltage of the input waveform. The levels of peaks in the signal can be shifted using the clamper circuit, hence clampers can also be referred as level shifters. Clampers can be broadly classified into two types. They are positive clampers and negative clampers.

1. **Positive Clamper:** This type of clamping circuit shifts the input waveform in the positive direction, as a result the waveform lies above a DC reference voltage.



2. **Negative Clamper:** This type of clamping circuit shifts the input waveform in the negative direction, as a result the waveform lies below a DC reference voltage.

The direction of the diode in the clamping circuit determines the type of clamper circuit. The operation of a clamping circuit is mainly based on the switching time constants of the capacitor. However, capacitor in the circuit charges through the diode and discharges through the load.

(a) Negative Clamper

The Negative Clamping circuit consists of a diode connected in parallel with the load (fig. 1.18) The capacitor used in the clamping circuit can be chosen such that it must charge very quickly and it should not discharge very drastically. The anode of the diode is connected to the capacitor and cathode to the ground. During the positive half cycle of the

 


Fig. 1.18

input, the diode is in forward bias and as the diode conducts the capacitor charges very quickly. During the negative half cycle of the input, the diode will be in reverse bias and the diode will not conduct, the output voltage will be equal to the sum of the applied input voltage and the charge stored in the capacitor during reverse bias. The output waveform is same as input waveform, but shifted below 0 volts.



(b) Negative Clamper with Positive Reference Voltage

The circuit arrangement is very similar to the negative clamper circuit, but a DC reference supply is connected in series with the diode (fig. 1.19). The output waveform is also similar to the negative clamper output waveform, but it is shifted towards the negative direction by an amount equal to the reference voltage at the diode.

 


Fig. 1.19

c) Negative Clamper with negative reference voltage

If the reference voltage directions in the above circuit are reversed (fig. 1.20) and connected to the diode in series, then during the positive half cycle the diode starts conducting current before applying input voltage. Since the cathode has a very small negative reference voltage less than zero volts, the waveform is shifted away from the 0 volts towards the negative direction by an amount of the reference voltage.

 


Fig. 1.20



1.17 Positive Clamper

The circuit of the positive clamper is similar to the negative clamper but the direction of the diode is inverted in such a way that the cathode of the diode is connected to the capacitor (fig. 1.21)

 


Fig. 1.21

During the positive half wave cycle, output voltage of the circuit will be the sum of applied input voltage and the charge stored at capacitor. During the negative half wave cycle, the diode starts to conduct and charges the capacitor very quickly to its maximum value. The output waveform of the positive clamper shifts towards the positive direction above the 0 volts.

(a) Positive Clamper with Positive Reference Voltage

A positive reference voltage is connected in series with the diode in the positive clamper circuit (fig. 1.22) such that the positive terminal of the reference voltage is connected in series with the anode of the diode. During the positive half wave cycle of the input sinusoidal waveform, the diode starts conducting, because initially the supply voltage is less than the diode's anode positive reference voltage. If once the cathode voltage is greater than anode voltage, the diode stops conduction of electric current. During the negative half cycle, the diode conducts and charges the capacitor very quickly.

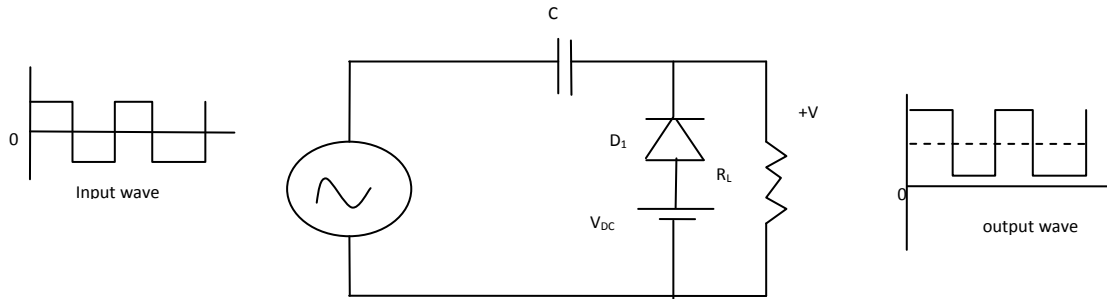


Fig. 1.22

(b) Positive Clamper with Negative Reference Voltage

The direction of the reference voltage is reversed in this case (fig. 1.23) such that the negative terminal of the reference voltage is connected in series with the anode of diode reflecting it as a negative reference voltage. During the positive half wave cycle of the input waveform, the diode does not conduct, as a result the output is equal to voltage stored in the capacitor and applied input voltage. During the negative half cycle, the diode starts conducting current after the cathode voltage value is less than the anode voltage and we get the waveform as shown.

 


Fig. 1.23

1.18 Features of clamping circuits

- 1) The shape of the waveform will be the same, but its level is shifted either upward or downward direction.



- 2) There will be no change in the peak-to-peak or rms value of the waveform due to the clamping circuit.
- 3) There will be a change in the peak and average values of the waveform.
- 4) The values of the resistor R and capacitor C affect the waveform.
- 5) The values for the resistor R and capacitor C should be determined from the time constant equation of the circuit, $t = RC$. In a good clamper circuit, the circuit time constant $T = RC$ should be at least ten times the time period of the input signal voltage.

1.19 Uses

- 1) Clamping circuits are often used in television receivers as dc restorers.
- 2) They are used in analogue video processing to define portions of luminance wave form (black level)
- 3) They are used in Method of modulating AM transmitters
- 4) Clamping circuits are sometimes used in the bias circuits of oscillators or in automatic gain control (AGC) circuits.
- 5) Clampers are widely used in test equipments and other sonar systems.



UNIT II : TRANSISTORS AND AMPLIFIERS

Transistors – Transistor action – three modes of connection – biasing – load line and Q – point – voltage divider bias – stabilization – CE amplifier.

2.1 TRANSISTORS

The transistor is the fundamental building block of modern electronic devices. It is a semiconductor device used to amplify or switch electronic signals and electrical power. It is composed of semiconductor material usually with at least three terminals for connections. Voltage or current applied to one pair of the transistor's terminals changes the current through another pair of terminals. Because the controlled output power can be higher than the controlling input power, a transistor amplifies a given signal. The symbols used for a transistor are shown in the fig. 2.1. A transistor has three regions namely, Emitter, Base and Collector. Base region is the thinnest of all. Collector is wider than both Emitter and Base.

 


Fig. 2.1

Emitter is heavily doped so that it can eject large amount of charge carriers. Base is lightly doped so that it passes most of the charge carriers into collector. The collector is moderately doped.

Transistor Biasing

Transistor Biasing is the process of setting a transistor to dc operating voltage or current conditions to the correct level so that any ac input signal can be amplified correctly by the transistor. Establishing the correct operating point requires the proper selection of bias



resistors and load resistors to provide the appropriate input current and collector voltage conditions. The correct biasing point for a bipolar transistor, either npn or pnp, generally lies somewhere between the two extremes of operation with respect to it being either “fully-ON” or “fully-OFF” along its load line. This central operating point is called the *Quiescent Operating Point*, or *Q-point* for short. With a single resistor usage, the biasing voltages and currents do not remain stable during transistor operation and can vary enormously. Also the temperature of the transistor can adversely affect the operating point.

2.2 Bias Stabilisation

It should be ensured that the operating point of a transistor is fixed at a suitable point. If it is shifted then the transistor will be driven to undesired regions and the circuit will become unreliable. The following are the reasons for the shift of operating point.

- i. Variation of transistor parameters with temperature
- ii. Parameter change from one transistor to another.

Collector current produces heat at base-collector junction. This will increase the number of minority charge carriers at the reverse biased B-C junction and the leakage current increases. This in turn will increase the collector current. The cycle repeats again. So, the transistor will reach the saturation region. The excess heat produced sometimes damage the transistor. This situation is called *thermal runaway*.

Stability factor

Stability factor is defined as the rate of change of collector current with respect to collector leakage current keeping the current gain β and base current I_B constant.

$$\text{ie. Stability factor } S = \left(\frac{dI_C}{dI_{co}} \right)_{\beta, I_B} \quad (2.1)$$

where I_{co} is the collector leakage current.

2.3 Expression for Stability factor for C.E. configuration:

In C. E. configuration,



$$\text{Collector current } I_c = \beta I_B + (\beta + 1)I_{co}$$

Differentiating w.r.t. I_c , we can write

$$1 = \beta \frac{dI_B}{dI_c} + (\beta + 1) \frac{dI_{co}}{dI_c}$$

$$\text{But stability factor } S = \left(\frac{dI_c}{dI_{co}} \right)_{\beta, I_B}$$

$$\therefore 1 = \beta \frac{dI_B}{dI_c} + (\beta + 1) \frac{1}{S}$$

$$\text{or } (\beta + 1) \frac{1}{S} = 1 - \beta \frac{dI_B}{dI_c}$$

$$\text{or } S = \frac{\beta + 1}{1 - \left(\beta \frac{dI_B}{dI_c} \right)} \quad (2.2)$$

2.4 Fixed bias

Using a suitable resistance across the base of a transistor (fig. 2.2) a fixed amount of current may be passed through the base and hence this is called a fixed bias. In this circuit a resistance R_B is connected between the base and the positive terminal of the supply V_{CC} . Applying Kirchoff's voltage law to the base-emitter-ground loop we get,

$$V_{CC} = I_B R_B + V_{BE}$$

Where I_B is the base current and V_{BE} the base emitter voltage. From the above eqn.

$$I_B R_B = (V_{CC} - V_{BE}) \quad \text{or} \quad I_B = (V_{CC} - V_{BE}) / R_B \quad (2.3)$$

$= V_{CC} / R_B$, if V_{BE} is very small. Since the supply voltage V_{CC} , base resistor R_B are fixed, the base current is also fixed.

 


Fig.2.2



Advantages

- 1) It is a simple circuit to construct
- 2) The biasing conditions can be easily achieved
- 3) Since there is no resistance between base and emitter, no loading of the source by the biasing current is reached

Disadvantages

- 1) Stability factor is high resulting in quick thermal runaway
- 2) Poor stabilisation

2.5 Voltage divider biasing

The voltage divider is formed using external resistors R_1 and R_2 (fig. 2.3). The voltage across R_2 forward biases the emitter junction. By proper selection of resistors R_1 and R_2 , the operating point of the transistor can be made independent of feedback factor β . In this circuit, the voltage divider holds the base voltage fixed independent of base current provided the divider current is large compared to the base current. From the circuit,

$$I_1 = \frac{V_{CC}}{R_1 + R_2}$$

Voltage dropped across R_2 is given by

$$V_2 = \left(\frac{V_{CC}}{R_1 + R_2} \right) R_2$$

Using Kirchoff's voltage law to the base circuit,

 


FIG. 2.3



$$\begin{aligned}V_2 &= V_{BE} + V_E \\ &= V_{BE} + I_E R_E \\ \text{or } I_E &= \frac{V_2 - V_{BE}}{R_E}\end{aligned}$$

$$\text{Or } I_C = \frac{V_2 - V_{BE}}{R_E} \text{ since, } I_E = I_C$$


Thus, I_C is independent of transistor parameters and hence good stabilisation is ensured. This is the universal method providing transistor biasing.

Advantages of voltage divider biasing circuits

- 1) Only one dc supply is necessary.
- 2) Operating point is almost independent of β variation.
- 3) Operating point is stabilized against shift in temperature.

 2.6 Transistor action

Transistor operation is basically the action of a relatively small emitter-base bias voltage controlling a relatively large emitter-to-collector current. The current flow in the external circuit is always due to the movement of free electrons. The



nnp- transistor

Fig. 2.4

The transistor can be considered as two p-n junctions that are placed back to back. The structure has two p-n junctions with a narrow base region between collector and emitter. In normal operation, the base emitter junction is forward biased and the base collector junction is reverse biased. When a current flows through the base emitter junction, a current also flows in the collector circuit. This is larger and proportional to the one in the base circuit. In order to explain the way in which this happens, the example of an n-p-n transistor is taken. The same principles is used for the p-n-p transistor except that the current carrier is holes and the voltages are reversed.



The emitter in the n-p-n device is made of n-type material and here the majority carriers are electrons. When the base emitter junction is forward biased the electrons move from the n-region towards the p-region and the holes move towards the n-region. This enables a current to flow across the junction. When the junction is reverse biased the holes and electrons move away from one another resulting in a depletion region between the two areas and no current flows.

Operation of a bipolar junction transistor

When a current flows between the base and emitter, electrons leave the emitter and flow into the base. Normally the electrons would combine when they reach this area. However the doping

level in this region is very low and the base is also very thin. This means the most of the electrons are able to travel across this region without recombining with the holes. As a result the electrons migrate towards the collector, because they are attracted by the positive potential. In this way they are able to flow across and current flows in the collector circuit. It is found that the collector current is significantly higher than the base current, and because the proportion of electrons combining with holes remains the same the collector current is always proportional to the base current. In other words varying the base current

varies the collector current. The ratio of the base to collector current $\left(\frac{I_B}{I_C}\right)$ is given the

Greek symbol β . Typically the ratio β may be between 50 and 500 for a small signal

transistor. The ratio between collector current and emitter current $\left(\frac{I_C}{I_E}\right)$ is called α of the

transistor and the ratio between collector current and base current $\left(\frac{I_C}{I_B}\right)$ is called β of the

transistor.

 


Fig. 2.5



2.7 Relation between α and β of a transistor

The sum of base current and collector current is equal to the emitter current.

$$\text{ie. } I_E = I_B + I_C \quad \text{or} \quad I_C = I_E - I_B$$

$$\begin{aligned} \text{From definition } \alpha &= \left(\frac{I_C}{I_E} \right) = \left(\frac{I_E - I_B}{I_E} \right) \\ &= \frac{(I_E/I_C) - (I_B/I_C)}{(I_E/I_C)} = \frac{(1/\alpha) - (1/\beta)}{(1/\alpha)} \end{aligned}$$

cross multiplying,


$$\begin{aligned} \alpha \left(\frac{1}{\alpha} \right) &= \left(\frac{1}{\alpha} \right) - \left(\frac{1}{\beta} \right) \\ \text{or } \left(\frac{1}{\alpha} \right) - \left(\frac{1}{\beta} \right) &= 1 \end{aligned} \tag{2.4}$$

2.8 Different modes of connections

There are three basic configurations of transistors namely, Common Base (CB), Common Emitter (CE) and Common Collector (CC) modes used in electronic circuits. Some important characteristics of these different modes or configurations are given below. Based on these they are used for different applications. Figure (2.6) depicts all the three transistor configurations used in various applications of electronic circuit.

 (i) Common Base (C.B.) Mode

Common base mode (fig. 2.6a) is usually used for VHF and UHF amplifiers where, although the voltage gain is not high, there is little chance of the output signal being fed back into the input circuit. Because the base of the transistor is connected to ground in this mode, it forms an effective grounded screen between output and input. As the collector current in this mode is the emitter current minus the base current, the current gain (h_{fb} in common base mode) is less than unity.



Characteristics

- It has low input impedance (on the order of 50 to 500 Ohms).
- It has high output impedance (on the order of 1 to 10 Mega Ohms).
- Current gain (α) is less than unity.

(ii) Common Emitter (C.E) mode

The most common function of a transistor is the common emitter mode (fig. 2.6b). In this method of connection small changes in base or emitter current cause large changes in collector or emitter current. Therefore the circuit is that of a current amplifier. To give voltage amplification, a load resistor must be connected in the collector circuit, so that a change in collector current causes a change in the voltage developed across the load resistor. The output waveform will be 180 degree out of phase to the input waveform.

Characteristics

- It has high input impedance (on the order of 500 to 5000 Ohms).
- It has low output impedance (on the order of 50 to 500 Kilo Ohms).
- Current gain (β) is 98.
- Power gain is upto 37 dB.
- Output is 180 degree out of phase.

(iii) Transistor Common Collector (C. C) mode

The C.E. mode also called the emitter follower is shown in the fig. 2.6(c). The output waveform at the emitter is not inverted and so follows the input waveform at the base.



This method of connection is often used as a buffer amplifier for such jobs as matching impedances between two other circuits. This is because this mode gives the amplifier a high input impedance and a low output impedance. The voltage gain in this mode is slightly less than unity, but high current gain is available. Another use for this mode of connection is a current amplifier, often used for output circuits that have to drive high current AC devices such as loudspeakers or DC devices such as motors etc.

Characteristics

1. It has high input impedance (on the order of about 150 to 600 Kilo Ohms).
2. It has low output impedance (on the order of about 100 to 1000 Ohms).
3. Current gain (β) is about 99.
4. Voltage and power gain is equal to or less than one.

Following table summarizes important points about CB, CE, CC transistor configurations.

Comparison between C.E., C.B., C.C. connections of a transistor

Parameter	C.B	C.E	C.C
Voltage Gain	High, same as CE	High	Less than Unity
Current Gain	Less than Unity	High	High
Power Gain	Moderate	High	Moderate
Phase inversion	No	Yes	No
Input Impedance	Low (50 Ω)	Moderate(1K Ω)	High (300 K Ω)
Output Impedance	High (1 M Ω)	Moderate (50 K Ω)	Low (300 Ω)



2.9 Transistor Static characteristics in C.E mode

The basic circuit diagram for studying the characteristics of a given transistor is shown in the fig. 2.7. The input is applied between base and emitter, the output is taken between collector and emitter. Here the emitter of the transistor is common to both input and output and hence called CE mode. Input characteristics are obtained between the input current and input voltage at constant output voltage (V_{CE}). It is plotted between V_{BE} and I_B at constant V_{CE} in CE configuration. Output characteristics are obtained between the output voltage and output current at constant input current (I_B). It is plotted between V_{CE} and I_C at constant I_B in CE configuration.

Experiment

Input Characteristics

Connections are made as shown in the circuit diagram (fig. 2.7). Output voltage is kept at $V_{CE} = 0V$ by varying the rheostat (R_{h2}). By using the rheostat (R_{h1}), V_{BE} is gradually varied and the base current I_B and base-emitter voltage V_{BE} are noted. Initially V_{BE} is varied in steps of 0.1 V. Once the current starts increasing it is varied in steps of 1V up to 12V. The procedure is repeated for $V_{CE} = 2V, 3V$ etc.

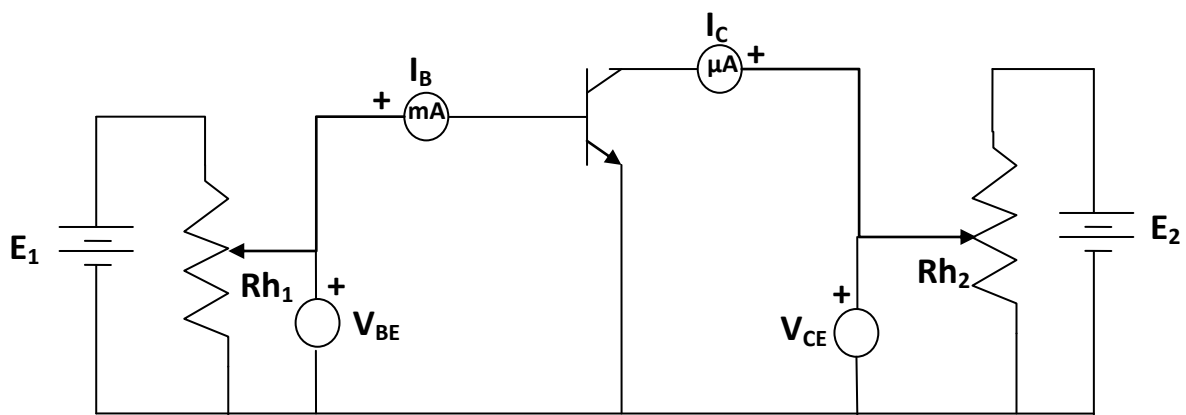


Fig. 2.7

Output Characteristics

To study the output characteristics, base current is fixed at (say) $I_B = 20 \mu A$. V_{CE} is gradually varied in steps of 1V up to 12V and collector current I_C and Collector-Emitter Voltage V_{CE} are noted. This procedure is repeated for $I_B = 40 \mu A, 60 \mu A$, etc. The readings are



tabulated as shown and suitable graphs are drawn. The various parameters related are calculated using the following formula


$$\text{Input resistance } r_i = \left(\frac{\Delta V_{BE}}{\Delta I_B} \right)_{V_{CE}}$$

$$\text{Output resistance } r_o = \left(\frac{\Delta V_{CE}}{\Delta I_C} \right)_{I_B}$$

$$\text{Current gain } \beta = \left(\frac{I_C}{I_B} \right)_{V_{CE}} \quad (2.5)$$

Input Characteristics


V _{CE} =1V		V _{CE} =2V		V _{CE} =3V	
V _{BE} (Volts)	I _B (μA)	V _{BE} (Volts)	I _B (μA)	V _{BE} (Volts)	I _B (μA)

 

(a)

Output Characteristics

I _B =0 μA		I _B =20 μA		I _B =40 μA	
V _{CE} (Volts)	I _C (mA)	V _{CE} (Volts)	I _C (mA)	V _{CE} (Volts)	I _C (mA)

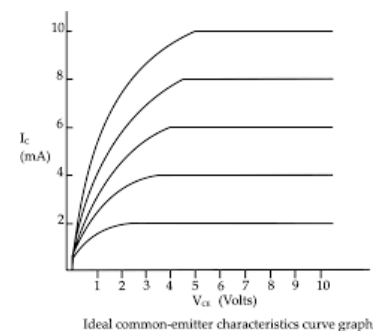

(b)

Fig. 2.8

2.10 Quiescent Point (Q-Point)

In an amplifier to get faithful amplification, suitable bias resistance and voltage values must be selected for the given transistor. This condition gives a set of d.c. voltage and current values in the transistor under zero signal condition. This is known as the *operating point* or *Q- point*. It is a point on the dc load line which represents dc collector – emitter voltage



(V_{CE}) and collector current (I_C) in the absence of ac signal. It is also called the operating point because the variations in V_{CE} and I_C take place about this point when signal is applied. The best position for this point is midway between cut-off and saturation points where $V_{CE} = 1/2 V_{CC}$. Q - Point marked on the output characteristics curve. Q-point shifts up and down along the ac load line when changes in output voltage and current of an amplifier are caused by an ac signal

Significance of Q - point in transistor

Normally whatever signals we want to amplify will be of the order milli volts or less. If we directly input these signals to the amplifier they will not get amplified as transistor needs voltages greater than cut in voltages for it to be in active region. Only in active region of operation transistor acts as amplifier. So we can establish appropriate DC voltages and currents through transistor by external sources so that the transistor operates in active region and superimpose the AC signals to be amplified. The DC voltage and current are so chosen that the transistor remains in active region for entire AC signal. All the input AC signals variations happen around Q-point. The points where the characteristic curve and the load line intersect are the possible operating points or Q points. To maintain the transistor at Q value for all operating signal values, suitable biasing is done.

2.11 Load line analysis

To draw DC load line of a transistor, we need to find the saturation current and cutoff voltage. The saturation current is the maximum possible current through the transistor and occurs at the point where the voltage across the collector is minimum. The cutoff voltage is the maximum possible voltage across the collector and occurs at zero collector current. A common emitter amplifier circuit is shown in the fig. 2.9(a). When collector current $I_C=0$, the collector-emitter voltage is maximum and is equal to V_{CC} .

$$\text{Maximum } V_{CE} = V_{CC} - R_C I_C$$

$$\therefore (V_{CE})_{\max} = V_{CC} \text{ since, } I_C = 0 \quad 2.6(b)$$

This gives the cut off point ($V_{CE}, 0$) on X-axis [fig. 2.9(b)]



When collector emitter voltage $V_{CE} = 0$, the collector current is maximum and is equal to V_{CC} / R_C .

$$\therefore 0 = V_{CC} - I_C R_C$$

$$\text{Maximum } I_C = V_{CC} / R_C$$

This gives the cut off point on Y-axis. Joining these two points gives the dc load line.

 


Fig. 2.9

Operating point

The zero signal values of I_C and V_{CE} are known as operating point. The variations of I_C and V_{CE} take about this point when signal is applied. Let, in the absence of signal the base current is $10 \mu A$. Then I_C and V_{CE} condition are represented by some point on dc load line AB. Q-point is the point where the load line and the characteristic curve intersect

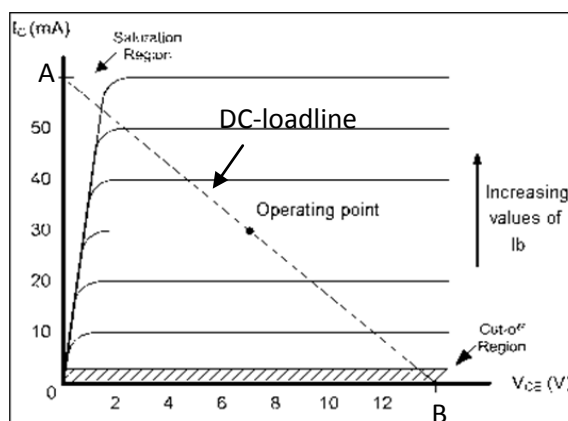


Fig. 2.10



2.12 CE Amplifier

In electronics, a common emitter amplifier is one of the three basic single-stage bipolar-junction-transistor (BJT) amplifier topologies, typically used as a voltage amplifier. In this circuit, the base terminal of the transistor serves as the input, the collector is the output and the emitter is common to both.

Construction

A basic C.E. transistor amplifier circuit using a pnp transistor is shown in the fig. (2.11). R_1 and R_2 form the potential divider biasing for the transistor. To compensate the variation of collector current, a resistance R_E is connected at the emitter. To eliminate the variation of voltage across R_E , a capacitor C_E is connected parallel to R_E . C_s prevents any dc flow into the input. C_c is the coupling capacitor to the next stage.

Working:

When an ac input signal is applied at the base, the output is obtained at the collector across the load R_L . There is a phase change of 180 degree between the input and output of this amplifier. For example, if the input signal increases it induces a small increase in base current. This will cause a

large change in collector current due to transistor action. This large change in collector current causes a large change in voltage across the load. Thus a weak signal is amplified at the output. We can draw a series of curves that show the

 


Fig. 2.11

Collector current, I_c against the Collector-Emitter voltage (V_{CE}) with different values of base current, I_b . These curves are known as the Output Characteristic Curves and are used to show how the transistor will operate over its dynamic range. When the transistor is switched "OFF", V_{CE} equals the supply voltage V_{CC} and this is point B on the line. Likewise



when the transistor is fully “ON” and saturated the Collector current is determined by the load resistor, R_L and this is the point A on the line. Point Q on the load line gives the base current. As the load line cuts through the different base current values on the DC characteristics curves we find the peak swings of base current that are equally spaced along the load line. These values are marked as points L and M on the line, Any input signal giving a base current greater than this value will drive the transistor to go beyond point M and into its “cut-off” region or beyond point L and into its saturation region thereby resulting in distortion to the output signal in the form of “clipping”. Using points L and M as an example, the instantaneous values of collector current and corresponding values of collector-emitter voltage can be projected from the load line. It can be seen that the collector-emitter voltage is in anti-phase (-180°) with the collector current. As the base current I_B changes in a positive direction the collector-emitter voltage, or the output voltage decreases from its steady state value. Thus a single stage Common Emitter Amplifier is also called an inverting amplifier.

 


Fig. 2.12

2.13 Frequency response curve

The variation of the gain of the amplifier with frequency is shown in the fig. 2.12. This response is called frequency response curve. At low frequencies of the input signal, the gain increases. In the middle range it is constant. At high frequency range the gain again

 


Fig. 2.13

decreases. 0.707 times the maximum gain value cut the curve at two points called low cutoff (f_1) and high cut off (f_2) frequencies. (f_2-f_1) gives the bandwidth of the amplifier.

Special features of CE amplifier

1. Input impedance is low
2. Output impedance is high
3. Input and out are 180 degree out of phase
4. Voltage gain and current gains are high



UNIT III : OSCILLATORS

Principles of negative voltage feed back in amplifiers – gain – advantages – principle of negative current feedback – Oscillation – Bark Hausen criterion for oscillation – colpitt's oscillator

3.1 Feedback Circuits

Feedback loops are used to control the output of electronic circuits. A feedback loop is created when all or some portion of the output is fed back to the input. There are two types of feedback circuits. They are positive feedback circuits and negative feedback circuits.

(i) Negative feedback

A negative feedback circuit is an electronic circuit that subtracts a fraction of its output from its input, so that it opposes the original signal. The applied negative feedback improves the performance by the ways of gain stability, linearity, frequency response, step response and reduces sensitivity to parameter variations due to manufacturing or environment. Because of these advantages, many amplifiers and control systems use negative feedback.

(ii) Positive feedback

When the feedback energy which may be voltage or current, is in phase with the input signal then it is called positive feedback. In this case, both amplifier and the feedback circuit introduce each a phase shift of 180° . The net result is 360° phase shift around the loop.

3.2 Effect of negative feed back

Let V_0 be the output voltage and V_i is the input voltage of an amplifier.

$$\text{Then the gain of the amplifier is } A = \frac{V_0}{V_i}. \quad (3.1)$$

Now using a feedback network, let a fraction of the output (β) is fed back to the input.

$$\text{Now the total input voltage is } V_i = V_s + \beta V_0 \quad (3.2)$$

From eqn 3.1,

$$V_0 = AV_i \quad \text{or} \quad V_i = \frac{V_0}{A}$$



Substituting this in eqn. (3.2), we get

$$\begin{aligned}\frac{V_0}{A} &= V_s + \beta V_0 \\ V_0 &= AV_s + A\beta V_0 \\ V_0(1 - A\beta) &= AV_s \\ \frac{V_0}{V_s} &= A' = \frac{A}{1 - A\beta}\end{aligned}\tag{3.3}$$

This gives the gain of the amplifier with feedback.

If the feed back fraction β is negative then the gain with negative feedback is,

$$A' = \frac{A}{1 + A\beta}. \quad \text{That is } A' < A. \quad \text{This means}$$

the gain decreases with negative feedback.

If the feedback fraction β is positive, then

$$A' = \frac{A}{1 - A\beta}. \quad \text{That is } A' > A \text{ or the gain increases with positive feedback.}$$

 


Fig. 3.1

If $A\beta=1$, then $A' = \frac{A}{1 - A\beta} = \infty$. That is the gain becomes infinite. In other words

there is output even if there is no input. This forms an oscillator. The amplifier introduces a phase difference of 180° . If the feedback network produces another phase difference of 180° , totally there will be a phase difference of 360° . This kind of feed back is called regenerative feedback. So, the conditions for continuous oscillations may be stated as,

1. the feed back factor $A\beta=1$
2. feedback must be positive

The above conditions are called *Barkhausen criterion* for oscillation.

3.3 Advantages of negative feedback amplifier

1. **Gain stability:** The negative feedback amplifier increases the Gain Stability. The gain will be stable over external or internal variations.



2. **Noise reduction:** By using negative feedback amplifier we can reduce the noise level to some extent
3. **Increase of Bandwidth:** Negative feedback amplifier decreases the Voltage gain, the reduction in voltage gain results improved Frequency Band Width.
4. **Increase in input impedance:** The amplifier with negative feedback Increases the Input impedance. Thus we can avoid loading of signal source.
5. **Decrease in output impedance:** Negative feedback decreases its output impedance

Problem: The gain of an amplifier is 120. When negative voltage feedback is applied, the gain is reduced to 20. Find the feedback ratio?

Given: $A = 120$; $A' = 20$; $\beta = ?$

We know that the gain of an amplifier with negative feedback is $A' = \frac{A}{1 + A\beta}$

Substituting the values,

$$20 = \frac{120}{1 + 120\beta} \quad \text{or} \quad 20 + 2400\beta = 120$$

$$\text{Or } \beta = \frac{100}{2400} = \frac{1}{24}$$

$$\text{So, the feedback ratio} = \frac{1}{24}$$

3.4 Effect of negative feedback on the stability of an amplifier

Eventhough the negative feedback reduces the gain of an amplifier, it increases the stability.

Consider an amplifier with negative feedback. Its closed loop gain is given by



$$A' = \frac{A}{1 + A\beta} \quad (3.4)$$

If feedback fraction β is very large, then we can assume $1 + A\beta = A\beta$

From eqn. (3.4),
$$A' = \frac{A}{1 + A\beta} = \frac{A}{A\beta} = \frac{1}{\beta} \quad (3.5)$$

So the gain is depending only on the feedback fraction β , which depends on feedback network, and is independent of any other amplifier parameters. Thus negative feedback improves the stability of the amplifier.

3.5 Feedback circuit

The network used for providing negative voltage feedback is shown in the fig. 3.2. It consists of a potential divider arrangement by using two resistors R_1 and R_2 . The output voltage of

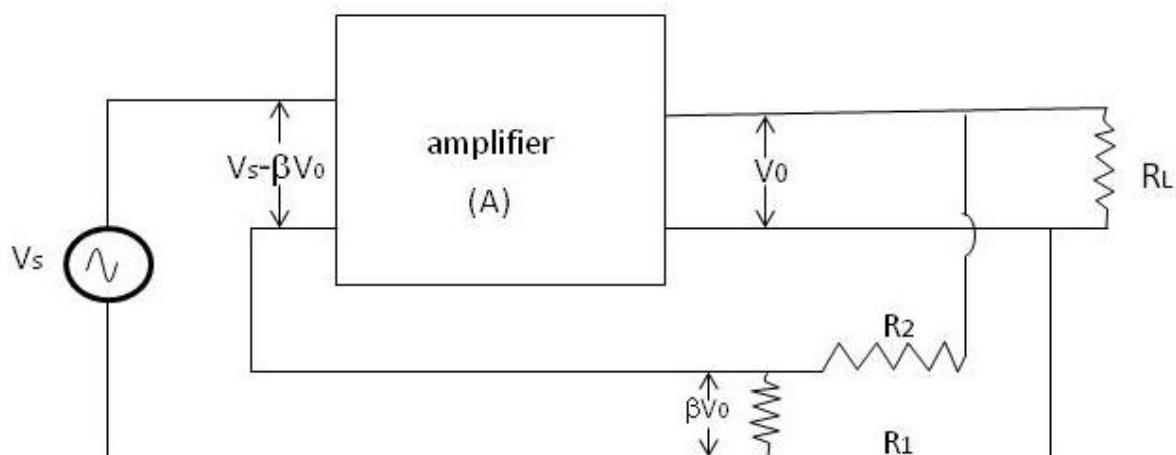


Fig. 3.2

the amplifier is fed across this arrangement. By choosing suitable values for the resistors, a required negative feedback is obtained.



From the circuit, voltage across $R_1 = \frac{V_0}{R_1 + R_2} \times R_1$

$$\text{Feedback fraction } \beta = \frac{\text{voltage across } R_1}{V_0} = \frac{R_1}{R_1 + R_2} \quad (3.6)$$

3.6 Principle of negative current feed back

In this method, a fraction of output current is feedback to the input of the amplifier. It is also called current-shunt feedback circuit. Let A_i be the gain of the amplifier without feedback. If I_i is the input current, then the output current can be expressed as

$I_{out} = A_i \times I_i$. Let a fraction m_i of the output current is feedback to the input through a resistance R_f .

Now, the feedback current $I_f = m_i I_{out}$

$$\text{Feedback fraction } m_i = \frac{I_f}{I_{out}} = \frac{\text{feedback current}}{I_{out}}$$

The negative current feedback reduces the input current to the amplifier and hence reduces the current gain

 


Fig. 3.3

3.7 Negative feedback amplifier circuit

Consider the circuit shown in the fig. 3.4. There is change in emitter current following the input signal. This emitter current I_e produces a voltage drop $I_e \times R_E$. When emitter current



increases with increase in signal voltage, the base-emitter voltage decreases which gives the required negative feedback

The net input after negative feedback is

$$V_{BE} = V_s - i_c R_E = V_s - i_c R_E, \text{ since } i_e = i_c \quad (3.7)$$

There is decrease in collector potential for increasing I_c

 


Fig. 3.4

$$V_0 = -i_c R_c \quad \text{or} \quad i_c = -\frac{V_0}{R_c}$$

Substituting this value in eqn. (3.5),

$$V_{BE} = V_s + V_0 \frac{R_E}{R_c} = V_s + V_0 \beta \quad \text{since} \quad \beta = R_E / R_c$$

$$\text{Or} \quad \frac{V_{BE}}{V_0} = \frac{V_s}{V_0} + \beta$$

$$\text{ie.} \quad \frac{1}{A'} = \frac{1}{A} + \beta$$

$$\frac{1}{A'} = \frac{1 + A\beta}{A} \quad \text{or} \quad A' = \frac{A}{1 + A\beta}$$

When the gain A is large so that $A\beta > 1$



$$A' = \frac{A}{A\beta} = \frac{1}{\beta}$$

The closed loop gain of the negative feedback amplifier is

$$A' = R_C / R_E$$

Problem: An amplifier has a gain of 100 without feedback. If a negative feedback with feedback ratio of 0.1 is applied, find the new gain of the amplifier?

We know that, the gain of an amplifier with negative feedback is

$$A' = \frac{A}{1 + A\beta}. \text{ Here, } A = 100 \text{ and } \beta = 0.1$$

$$\therefore \text{ Gain with feedback } A' = \frac{A}{1 + A\beta} = \frac{100}{1 + (100 \times 0.1)} = \frac{100}{1 + 10} = \frac{100}{11} = 9.09$$

So, the new gain with feedback = 9.09

An amplifier has a gain of 100 without feedback. When negative feedback is applied the gain is reduced to 50. Find the feedback fraction.

Given: $A = 100$; $A' = 50$; $\beta = ?$

We know that the gain with negative feedback is $A' = \frac{A}{1 + A\beta}$

$$\begin{aligned} A'(1 + A\beta) &= A \\ \text{ie. } A'A\beta &= A - A' \\ \beta &= \frac{A - A'}{AA'} = \frac{100 - 50}{100 \times 50} = 0.01 \end{aligned}$$

3.8 Emitter Follower (Negative current feedback circuit)

The circuit shown in fig. 3.5 is the emitter follower circuit or common collector amplifier circuit. The ac voltage V_{in} is coupled into the base of the transistor through the coupling



capacitor (C_1). This ac signal rides on the DC base voltage or the Q point voltage. The ac signal appears at the emitter. This ac current signal produces a voltage across the emitter resistor R_E . The output is taken at the emitter by using coupling capacitor (C_2). R_L is the load resistor.

 


Fig. 3.5

The output voltage across the load resistor R_L is in phase with the input voltage. The output voltage follows the input voltage. The magnitude of the output voltage across the load resistor (R_L) is approximately equal to the magnitude of the input voltage. This is the reason why this common collector amplifier is called emitter follower.

The emitter resistor R_E gives a negative feedback. This negative feedback causes many effects. First this negative feedback causes stability of the gain, second it reduces distortion and third it increases the input impedance. In any of the design in which these features are required, emitter follower circuit can be used. It provides low impedance at the output. Because of the feature of high impedance at the input and low impedance at the output, emitter follower circuit is used as pre-amplifier. One of the application example is the driving an audio speaker. The audio speaker has low impedance and for maximum power transfer into the speaker, the emitter follower is connected to the speaker. The voltage gain of the emitter follower circuit is approximately equal to unity. That is emitter follower circuit



does not provide voltage gain. However it provides current gain and thereof power gain. Thus because of this current gain and power gain emitter follower is called an amplifier.

3.9 Oscillator

An electronic oscillator is a circuit that produces a periodic, oscillating electronic signal, often a sine wave or a square wave. Oscillators convert direct current (DC) from a power supply to an alternating current (AC) signal. They are widely used in many electronic devices. Common examples of signals generated by oscillators include signals broadcast by radio and television transmitters, clock signals that regulate computers and quartz clocks, and the sound produced by electronic beepers and video games.

Oscillators are characterized by the frequency generated at the output. They are,

- i. A low-frequency oscillator (LFO) is an electronic oscillator that generates a frequency below 20 Hz. This is used in the field of audio synthesizers, to distinguish it from an audio frequency oscillator.
- ii. An audio oscillator produces frequencies in the audio range, about 20 Hz to 20 KHz.
- iii. An RF oscillator produces signals in the radio frequency (RF) range of about 100 KHz to 100 GH

3.10 Essential requirements for an oscillator

- 1) **Amplifier:** which receives dc power from a dC source and convert it into ac power
- 2) **Tank circuit:** which consists of an inductor (L) and a capacitor (C) connected parallel to each other. The resonance frequency depends upon the values of L and C
- 3) **Feedback circuit:** A network providing a feedback of a fraction of the output back into the input. The feedback must be positive such that the feedback signal is in phase with the input signal.

3.11 Tank Circuit

A tank circuit or an oscillatory circuit is a parallel form of inductor and capacitor elements which produces the electrical oscillations of any desired frequency. Both these elements are capable of storing energy. Whenever the potential difference exists across a capacitor



plates, it stores energy in its electric field. Similarly, whenever current flows through an inductor, energy is stored in its magnetic field. The figure 3.6 shows a tank circuit in which inductor L and capacitor C are connected in parallel.

 


FIG. 3.6

Let us consider that the capacitor is initially charged with a DC source having the polarities upper plate positive and lower plate negative as shown (fig. 3.6). This represents that the upper plate has of electrons deficiency , whereas the lower plate has excess of electrons. Therefore, potential differences exist between these two plates. Consider that this charged capacitor is connected across the inductor. The conventional current flow from positive polarity to negative polarity through the inductor coil. Therefore the energy stored or strength of the electric field in the capacitor decreases. The current flowing through the inductor induces an e.m.f. which opposes the electrons flow through it. This current flow set up a magnetic field around the inductor thereby it starts storing the magnetic energy. When the capacitor is fully discharged, current through the coil becomes zero. At this time magnetic field has maximum value and there is no electric field. Thus the electrical energy is converted into magnetic energy.

Once the capacitor is fully discharged, magnetic field around the inductor starts collapsing and produces the counter e.m.f. As per the Lenz's law, this counter e.m.f. produces the current which begin to charge the capacitor with opposite polarity by making plate upper plate negative and lower plate positive as shown in figure. When the capacitor is fully charged in opposite direction, the entire magnetic energy is converted back into the electric energy in capacitor, i.e., magnetic energy is collapsed. At this instant, capacitor starts discharging in the opposite direction. Once again the capacitor is fully discharged and this process will be continued. This continuous charging and discharging process results in an alternating motion of electrons which is nothing but an oscillating current.



3.12 Feedback oscillator

The most common form of linear oscillator is an electronic amplifier such as a transistor or operational amplifier connected in a feedback loop with its output fed back into its input through a frequency selective electronic filter to provide positive feedback. When the power supply to the amplifier is first switched on, electronic noise in the circuit provides a non-zero signal to get oscillations started. The noise travels around the loop and is amplified. Feedback oscillator circuits can be classified according to the type of frequency selective filter they use in the feedback loop.

In an *RC oscillator* circuit, the filter is a network of resistors and capacitors. RC oscillators are mostly used to generate lower frequencies, for example in the audio range. Common types of RC oscillator circuits are the phase shift oscillator and the Wien bridge oscillator.

In an *LC oscillator* circuit, the filter is a tuned circuit, called a *tank circuit* consisting of an inductor (L) and capacitor (C) connected parallel to each other. Charge flows back and forth between the capacitor's plates through the inductor, so the tuned circuit can store electrical energy oscillating at its resonant frequency. There are small losses in the tank circuit, but the amplifier compensates for those losses and supplies the power for the output signal. LC oscillators are often used at radio frequencies when a tunable frequency source is necessary, such as in signal generators, tunable radio transmitters and the local oscillators in radio receivers. Typical LC oscillator circuits are the Hartley, Colpitts and Clapp circuits

In a *crystal oscillator* circuit the filter is a piezoelectric crystal (commonly a quartz crystal). The crystal mechanically vibrates as a resonator, and its frequency of vibration determines the oscillation frequency. Crystals have very high Q-factor and also better temperature stability than tuned circuits, so crystal oscillators have much better frequency stability than LC or RC oscillators. Crystal oscillators are the most common type of linear oscillator, used to stabilize the frequency of most radio transmitters, and to generate the clock signal in computers and quartz clocks. Crystal oscillators often use the same circuits as LC oscillators, with the crystal replacing the tuned circuit. Quartz crystals are generally limited to frequencies of 30 MHz or below. Other types of resonator, dielectric resonators and surface



acoustic wave (SAW) devices, are used to control higher frequency oscillators, up into the microwave range. For example, SAW oscillators are used to generate the radio signal in cell phones.

3.13 Colpitts Oscillator

Colpitts oscillator was invented by American scientist Edwin Colpitts in 1918. It is another type of sinusoidal LC oscillator. In Colpitts oscillator the tank circuit consists of two capacitors in series and an inductor connected in parallel to the serial combination. The frequency of the oscillations are determined by the value of the capacitors and inductor in the tank circuit. In Colpitts oscillator, the capacitive voltage divider setup in the tank circuit works as the feedback source and this arrangement gives better frequency stability when compared to the Hartley oscillator which uses an inductive voltage divider arrangement for feedback. The circuit diagram of a typical Colpitts oscillator using transistor is shown in the fig. 3.7.

In the circuit diagram resistors R_1 and R_2 provide a voltage divider biasing to the transistor. Resistor R_C limits the collector current of the transistor. C_i is the input DC decoupling capacitor while C_o is the output decoupling capacitor. R_E is the emitter resistor and its meant for thermal stability. C_E is the emitter by-pass capacitor. The emitter by-pass capacitor is to by-pass the amplified AC signals from dropping across R_E . Capacitors C_1 , C_2 and inductor L form the tank circuit. Feedback to the base of transistor is taken from the junction of Capacitor C_2 and inductor L in the tank circuit.

When the power supply is switched ON, capacitors C_1 and C_2 start charging. When they are fully charged they start discharging through the inductor L . When the capacitors are fully discharged, the electrostatic energy stored in the capacitors get transferred to the inductor as magnetic flux. The inductor starts discharging and capacitors get charged again. This transfer of energy back and forth between capacitors and inductor is the basis of oscillation. Voltage across C_2 is phase opposite to that of the voltage across the C_1 and it is the voltage across C_2 that is fed back to the transistor. The feedback signal at the base of transistor appears in the amplified form across the collector and emitter of the transistor. The energy lost in the tank circuit is compensated by the transistor and the oscillations are



sustained. The tank circuit produces 180° phase shift and the transistor itself produces another 180° phase shift. That means the input and output are in phase and it is a necessary condition of positive feedback for maintaining sustained oscillations. The frequency of oscillations of the Colpitts oscillator is determined using the equation,

$$F = \frac{1}{2\pi\sqrt{LC}}$$

where L is the inductance value of the inductor in the tank circuit and C is the effective

 


Fig. 3.7

capacitance of the capacitors in the tank circuit. If C_1 and C_2 are the individual capacitance, then the effective capacitance of the serial combination $C = C_1C_2/(C_1 + C_2)$. By using variable capacitors in place of C_1 and C_2 , the frequency of Colpitts oscillator can be made variable.



3.14 Condition for oscillation

The condition for the functioning of the oscillator is $A\beta > 1$. In the given circuit, voltage gain $A = R_c/r_e$, where R_c is the load resistance and r_e is the dynamic resistance of base emitter junction.

So the condition for oscillation is

$$\begin{aligned} \frac{R_c}{r_e} \beta &> 1 \\ \text{or } \frac{R_c}{r_e} &> \frac{1}{\beta} \end{aligned} \quad (3.7)$$

$$\text{Feedback ratio } \beta = \frac{\text{voltage feedback to the base}}{\text{output voltage}} = \frac{V_f}{V_0} = \frac{i/C_1\omega}{i/C_2\omega} = \frac{C_2}{C_1}$$

Substituting in eqn. 3.7

$$\frac{R_c}{r_e} > \frac{C_1}{C_2}$$

Or $h_{fe} > \frac{C_1}{C_2}$ where $h_{fe} = \left(\frac{R_c}{r_e}\right)$ is called the forward current gain.

This is the condition for oscillation.

3.15 Expression for frequency

Resonance frequency is the oscillator frequency

At resonance, $X_C = X_L$. That is $\frac{1}{C\omega} = L\omega$ where $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$

$$\text{Or } \omega^2 = \frac{1}{LC} \text{ or } \omega = 2\pi f = \frac{1}{LC}$$

$$\text{Or } f = \frac{1}{2\pi\sqrt{LC}}$$

This is the frequency of the colpitt's oscillator.



3.16 Advantages of Colpitts oscillator

Main advantage of Colpitts oscillator over Hartley oscillator is the improved performance in the high frequency region. This is because the capacitors provide a low reactance path for the high frequency signals and thus the output signals in the high frequency domain will be more sinusoidal. Due to the excellent performance in the high frequency region, the Colpitts oscillator can be even used in microwave applications. Colpitts oscillator is generally used in RF applications and the typical operating range is 20KHz to 300MHz.

In a Colpitts oscillator, $C_1 = 0.01 \mu F$, $C_2 = 0.001 \mu F$ and $L = 100 mH$. Find its frequency of operation?

$$\text{Frequency of oscillation} \quad f = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{Here the effective capacitance } C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$$


$$\text{ie. } C = \frac{0.01 \times 10^{-6} \times 0.001 \times 10^{-6}}{0.01 \times 10^{-6} + 0.001 \times 10^{-6}} = 0.0009 \times 10^{-6} \text{ F}$$

$$\therefore f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times 3.14 \times \sqrt{100 \times 10^{-3} \times 9 \times 10^{-10}}} = 1.68 \times 10^4 \text{ Hz}$$

For the colpitt's oscillator circuit given in the fig. 3.8, find the operating frequency and feedback fraction

$$\text{Frequency of oscillation } f = \frac{1}{2\sqrt{LC}}$$
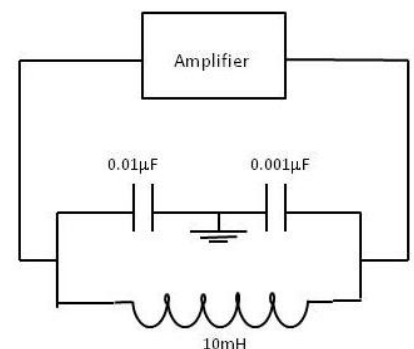
$$\text{Here } C = \frac{C_1 C_2}{C_1 + C_2}$$





In our problem,

$$L = 10 \times 10^{-3} H$$

$$C_1 = 0.001 \times 10^{-6} F \quad \text{and} \quad C_2 = 0.01 \times 10^{-6} F$$

Fig. 3.8

$$\therefore C = \frac{0.01 \times 10^{-6} \times 0.001 \times 10^{-6}}{0.01 \times 10^{-6} + 0.001 \times 10^{-6}} = 0.0009 \times 10^{-6}$$

$$\begin{aligned} \text{Hence, frequency of oscillation } f &= \frac{1}{2 \times 3.14 \sqrt{10 \times 10^{-3} \times 0.0009 \times 10^{-6}}} \\ &= 53100 Hz \end{aligned}$$

$$\text{Feedback fraction } \beta = \frac{C_1}{C_2} = \frac{0.001}{0.01} = \frac{1}{10}$$



UNIT IV : FIELD EFFECT TRANSISTOR

Principle , features and characteristics of FET – JFET and MOSFET – their characteristics – enhancement and depletion type

4.1 FIELD EFFECT TRANSISTOR

The field-effect transistor (**FET**) is a transistor that uses an electric field to control the flow of charges and hence the electrical conductivity of a channel of one type of charge carrier in a semiconductor material. There are two types of FET namely

1. Junction Field Effect Transistor
2. Metal Oxide Semi conductor Field Effect Transistor

FET has no PN-junctions but instead has a narrow piece of high resistivity semiconductor material forming a Channel of either N-type or P-type silicon for the majority carriers to flow through with two ohmic electrical connections at either end commonly called the Drain and the Source respectively. The applied gate voltage imposes an electric field into the device, which in turn attracts or repels charge carriers to or from the region between a source terminal and a drain terminal. The density of charge carriers in turn influences the conductivity between the source and drain. JFETs are working on the principle that the width and hence the resistance for the flow of charge carriers can be varied by changing the reverse voltage V_{GS}

Symbol used for FET is shown in the fig. 4.1.

The vertical line in the symbol may be thought as channel and source S and drain D connected to the line. The direction of the arrow at the gate indicates the direction in which the gate current flows when the gate junction is forward biased. Thus for the N-channel JFET, the arrow at the gate junction points into the device and in P-channel JFET, it is away from the device.

The FET has three terminals namely,

 


Fig. 4.1



1. Source (S), through which the carriers enter the channel. Conventionally, current entering the channel at S is designated by I_S .
2. Drain (D), through which the charge carriers leave the channel. Conventionally, current entering the channel at D is designated by I_D . Drain-to-source voltage is V_{DS} .
3. Gate (G), is the terminal that modulates the channel conductivity. By applying voltage to G, one can control I_D .

4.2 Difference between FET and Bipolar transistor

1. In FET, only one type of charge carrier (either electrons or holes) is used for conduction, so it is called unipolar device. In transistor, both types of charge carriers are used for conduction, hence called a bipolar device.
2. FET has high input impedance while a transistor has low input impedance
3. Almost zero current passes through the gate of a JFET. But in a transistor, a few μA of current pass through the base
4. FET uses gate voltage to control the output current while a transistor uses current through the base to control the output current. Hence we can say, a FET is characterised by its transconductance and the transistor is characterised by current gain.
5. Noise is less in FET because there are no junctions.

4.3 Construction of FET

There are two basic configurations of field effect transistor, the N-channel JFET (fig. 4.2 a) and the P-channel FET (4.2 b). The N-channel is doped with donor impurities meaning that the flow of current through the channel is negative (hence the term N-channel) in the form of electrons.

Likewise, the P-channel FET's channel is doped with acceptor impurities meaning that the flow of current through the channel is positive (hence the term P-channel) in the

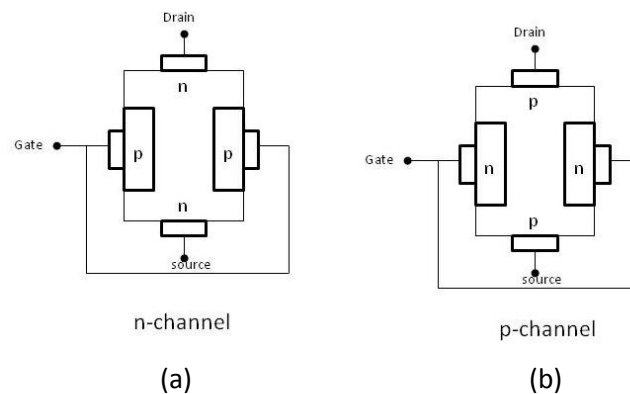


Fig. 4.2

form of holes. N-channel JFET's have a greater channel conductivity (lower resistance) than their equivalent P-channel types, since electrons have a higher mobility through a conductor compared to holes. This makes the N-channel JFET's a more efficient conductor compared to their P-channel counterparts. Within this channel there is a third electrical connection which is called the Gate terminal and this can also be a P-type or N-type material forming a PN-junction with the main channel.

In an n-channel FET an n-type silicon bar, referred to as the channel, has two smaller pieces of P-type silicon material diffused on the opposite sides of its middle part, forming P-N junctions, as illustrated in fig. 4.2 (a). The two P-N junctions forming diodes or gates are connected internally and a common terminal, called the gate terminal, is brought out. Ohmic contacts are made at the two ends of the channel, one lead is called the source terminal S and the other drain terminal D.

The silicon bar behaves like a resistor between its two terminals D and S. The gate terminal is analogous to the base of an ordinary transistor. It is used to control the flow of current from source to drain. Thus, source and drain terminals are analogous to emitter and collector terminals respectively of a junction transistor.

In figure 4.2(a) the gate is P-region, while the source and the drain are N-regions. Because of this, a JFET is similar to two diodes. The gate and the source form one of the diodes, and the



drain form the other diode. These two diodes are usually referred as the gate-source diode and the gate-drain diode. Since FET is a silicon device, it takes only 0.7 volts for forward bias to get significant current in either diode.

With the gate terminal not connected, and a potential applied (+ve at the drain and – ve at the source), a current called the drain current, I_D flows through the channel located between the two P-regions. This current consists of only majority carriers-electrons in this case. P-channel JFET is similar in construction to N-channel JFET except that P-type semiconductor material is sandwiched between two N-type junctions, as shown in figure. In this case majority carriers are holes.

Working

FET operation can be compared to that of a garden hose. The flow of water through a hose can be controlled by squeezing it to reduce the cross section and the flow of electric charge through a FET is controlled by constricting the current-carrying channel. The current also depends on the electric field between source and drain which is analogous to the difference in pressure on either end of the hose. Constriction of the conducting channel is accomplished using the field effect. A voltage between the gate and the source is applied to reverse bias the gate-source pn-junction, thereby widening the depletion layer of this junction .

4.4 Polarity conventions FET

The polarities for n-channel and p-channel JFET's are shown in figure. 4.3. In both of the cases the voltage between the gate and source is such that the gate is reverse biased. This is the normal method of connection of FETs. The drain and source terminals are penetrate more deeply into the channel at points lying closer to D than to S. Thus wedge-shaped depletion regions are formed, as shown in figure. when V_{DS} is applied. The size of the depletion layer formed determines-the width of the channel and hence the magnitude of current I_D flowing through the channel. interchangeable, that is either end can be used as a source and the other end as a drain. The source terminal is always connected to that end of

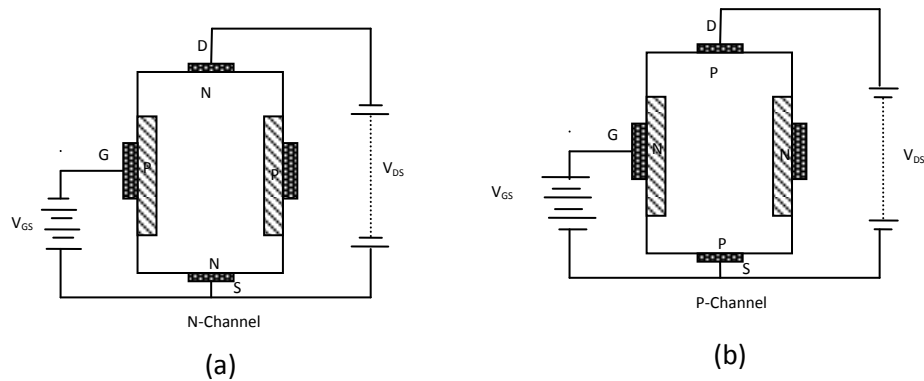


Fig. 4.3

the drain voltage supply which provides the necessary charge carriers, that is, in an N-channel JFET source terminal, S is connected to the negative end of the drain voltage supply.

4.7 Operation of FET

Consider the working of an n-channel FET .

(i)When no bias is applied to the gate (i.e. when $V_{GS} = 0$) or any voltage to the drain w.r.t. source (i.e. when $V_{DS} = 0$), the depletion regions around the P-N junctions , are of equal thickness and symmetrical.

(ii)When positive voltage is applied to the drain terminal D w.r.t. source terminal S, the electrons (which are the majority carriers) flow from terminal S to terminal D whereas conventional drain current I_D flows through the channel from D to S. Due to flow of this current, there is uniform voltage drop across the channel resistance as we move from terminal D to terminal S. This voltage drop reverse biases the diode. The gate is more negative with respect to those points in the channel which are nearer to D than to S. Hence, depletion layers get reduced causing decrease in resistance and , therefore, increase in drain current I_D . The gate-source voltage $(V_G)_{Sat}$ at which drain current I_D is cut-off completely (pinched off) is called the *pinch-off voltage* V_p . It is also to be noted that the amount of reverse bias is not the same throughout the length of the P-N junction. When the drain current flows through the channel, there is a voltage drop along its length.

 


Fig. 4.4

The result is that the reverse bias at the drain end is more than that at the source end making the width of depletion layer more at the drain. To see how the width of the channel varies with the variation in gate

4.8 Experiment to study Drain Characteristics and Transfer Characteristics of a Field Effect Transistor

The pin diagram (bottom view) of a FET is shown in the fig. 4.5. Drain characteristics are obtained between the drain to source voltage (V_{DS}) and drain current (I_D) taking gate to source voltage (V_{GS}) as the constant parameter. Transfer characteristics are obtained between the gate to source voltage (V_{GS}) and drain current (I_D) taking drain to source voltage (V_{DS}) as the constant parameter.

 


Fig. 4.5

Drain Characteristics: A circuit is connected as shown in the figure 4.6. Keeping $V_{GS} = 0V$, V_{DD} is gradually varied in steps of 1V up to 10V. The drain current I_D and drain to source voltage (V_{DS}) are noted. The above procedure is repeated for $V_{GS} = -1V$ and the readings are tabulated as shown in table.

 


FIG. 4.6

Transfer Characteristic

Setting $V_{DS} = 2V$, V_{GS} is varied in steps of $0.5V$ until the current I_D reduces to minimum value. By Varying V_{GS} gradually, both drain current I_D and gate-source voltage (V_{GS}) are noted. The above procedure is repeated for $V_{DS} = 4V/ 8V$ and the readings are tabulated . A graph is plotted by taking V_{DS} on X-axis and I_D on Y-axis at a constant V_{GS} . Transfer characteristics graph is plotted by taking V_{GS} on X-axis and taking I_D on Y-axis at constant V_{DS} .

 


Fig. 4.7



Drain Resistance (r_d): It is given by the relation of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in Drain Current (ΔI_D) for a constant gate to source voltage (ΔV_{GS}), when the JFET is operating in pinch-off region.

$$r_d = \left(\frac{\Delta V_{GS}}{\Delta I_D} \right) \text{ at a constant } V_{GS} \text{ (from drain characteristics)}$$

Trans Conductance (g_m): Ratio of small change in drain current (ΔI_D) to the corresponding change in gate to source voltage (ΔV_{GS}) for a constant V_{DS} .

$$g_m = \left(\frac{\Delta I_D}{\Delta V_{GS}} \right) \text{ at constant } V_{DS} \text{ (from transfer characteristics).}$$

The value of g_m is expressed in mho's (Ω).

Amplification factor (μ): It is given by the ratio of small change in drain to source voltage (ΔV_{DS}) to the corresponding change in gate to source voltage (ΔV_{GS}) for a constant drain current (I_D).

$$\mu = \left(\frac{\Delta V_{DS}}{\Delta V_{GS}} \right)_{I_D}$$

4.9 Relation between the FET parameters

Amplification factor $\mu = \frac{\Delta V_{DS}}{\Delta V_{GS}}$

Multiplying both the numerator and denominator by ΔI_D ,

$$\mu = \frac{\Delta V_{DS}}{\Delta V_{GS}} \times \frac{\Delta I_D}{\Delta I_D} = \frac{\Delta V_{DS}}{\Delta I_D} \times \frac{\Delta I_D}{\Delta V_{GS}} = r_d \times g_m$$
$$\therefore \mu = r_d \times g_m$$

This is the relation connecting the drain resistance, transconductance and amplification factor of a FET.

4.10 Advantages of FET

1. High degree of isolation between input and output circuits due to its very high input



impedance

2. Noise is highly reduced due to the absence of junctions
3. It has negative temperature coefficient. So the risk of thermal runaway is avoided.
4. It has high power gain which eliminates the uses of driving stages
5. It has High efficiency and longer life
6. It is relatively immune to radiation.
7. It exhibits no offset voltage at zero drain current and hence makes an excellent signal chopper.

4.11 Uses of FET

1. FET is suitable for switching analog signals between paths (multiplexing) due to its large input resistance and low output resistance,
2. it is effective as a buffer in common-drain (source follower) configuration.
3. It is used in switching internal combustion engine ignition coils, where fast switching and voltage blocking capabilities are important.

4.12 Some Definitions related with FET

Shorted gate drain current (I_{DSS}): It is defined as the drain current when the source is short circuited to gate ($V_{GS}=0$) and drain voltage (V_{DS}) equal to pinch off voltage. It is also called zero bias current.

Pinch off voltage (V_P): It is the minimum drain-source voltage at which the drain current becomes constant.

Gate-source cut off voltage $V_{GS(off)}$: It is the gate-source voltage where the channel is completely cut off and the drain current becomes zero.

4.13 MOSFET

MOSFET means Metal Oxide Semiconductor Field Effect Transistor. Metal (poly-silicon doped heavily - metal), Oxide (SiO_2 -an insulator), Semiconductor (n-type or p-type), Field



Effect (controlled by an electric field), Transistor (Three terminal device) are used here. There are two types of MOSFETS namely Depletion type MOSFET (D-MOSFET) and Enhancement type MOSFET (E-MOSFET). D-type can be operated in both depletion mode and enhancement mode but E-type can only be operated on enhancement mode only.

The n-channel D-MOSFET is a piece of n-type material with a p-type region called substrate on the right side and an insulated gate on the left as shown. The free electrons flowing from source to drain must pass through the narrow channel between the gate and the p-type region .

The Gate construction of D-MOSFET is explained as follows

A thin layer of metal oxide, usually silicon dioxide (SiO_2) is deposited over a small portion of the channel. A metallic gate is deposited over the oxide layer. As SiO_2 is an insulator, therefore, gate is insulated from the channel. The substrate is connected to the source internally so that a MOSFET has three terminals such as Source (S), Gate (G) and Drain(D). Since the gate is insulated from the channel, we can apply either negative or positive voltage to the gate. Therefore, D-MOSFET can be operated in both depletion-mode and enhancement-mode.

Again, there are two types of D-MOSFETs namely, n-channel D-MOSFET, p-channel D-MOSFET

n-channel D-MOSFET

Figure 4.8 shows the various parts of n-channel D-MOSFET. The p-type substrate constricts the channel between the source and drain so that only a small passage remains at the left side. Electrons flowing from source (when drain is positive w.r.t. source) must pass through this narrow channel. The symbol used for n-channel D-MOSFET is shown in fig. 4.9(a). The gate appears like a capacitor plate. Just to the right of the gate is a thick vertical line representing the channel. The drain lead comes out of the top of the channel and the source lead connects to the bottom. The arrow is on the substrate and points to the n-material, therefore we have n-channel D-MOSFET. The substrate is connected to the source as shown in fig. 4.9(b). This gives rise to a three terminal device.

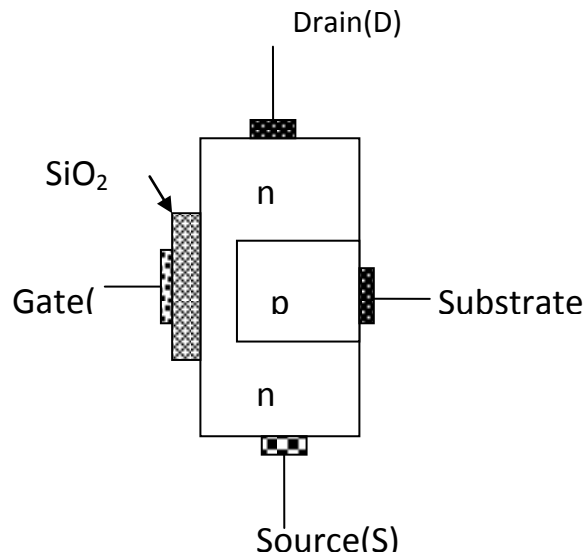


Fig.4.8

 


Fig. 4.9

p-channel D-MOSFET

Fig. 4.11 shows the various parts of p-channel D-MOSFET. The symbol for p-channel D-MOSFET is shown in fig.4.10(a). The source is connected to substrate internally as shown in fig.4.10(b). This results in a three-terminal device.

 


Fig. 4.10

 


Fig. 4.11

Circuit Operation of D-MOSFET

Fig. 4.12 shows the circuit of n-channel D-MOSFET. The gate forms a small capacitor. One plate of this capacitor is the gate and the other plate is the channel with metal oxide layer as the dielectric. When gate voltage is changed, the electric field of the capacitor changes which in turn changes the resistance of the n-channel. Since the gate is insulated from the channel, we can apply either negative or positive voltage to the gate. The negative gate operation is called *depletion mode* and positive gate operation is called *enhancement mode*.

1. Depletion mode

Figure 4.12 shows depletion mode operation of n-channel D-MOSFET. Since gate is negative, it means electrons are on the gate. These electrons repel the free electrons in the n-channel, leaving a layer of positive ions in a part of the channel as shown. In other words, the n-channel is depleted of some of its free electrons. Therefore, lesser number of free electrons are available for current conduction through the n-channel. The greater the negative voltage on the gate, the lesser is the current from source to drain. Thus by changing the negative voltage on the gate, we can vary the resistance of the n-channel and hence the current from source to drain. As the action with negative gate

 


Fig. 4.12

depends upon depleting the channel of free electrons, the negative-gate operation is called depletion mode.

2. Enhancement mode

Figure 4.13 shows enhancement mode operation of n-channel D-MOSFET. Again the gate acts like a capacitor. Since the gate is positive, it induces negative charges in the n-channel as shown in fig. 4.13 (b). These negative charges are the free electrons drawn into the channel.

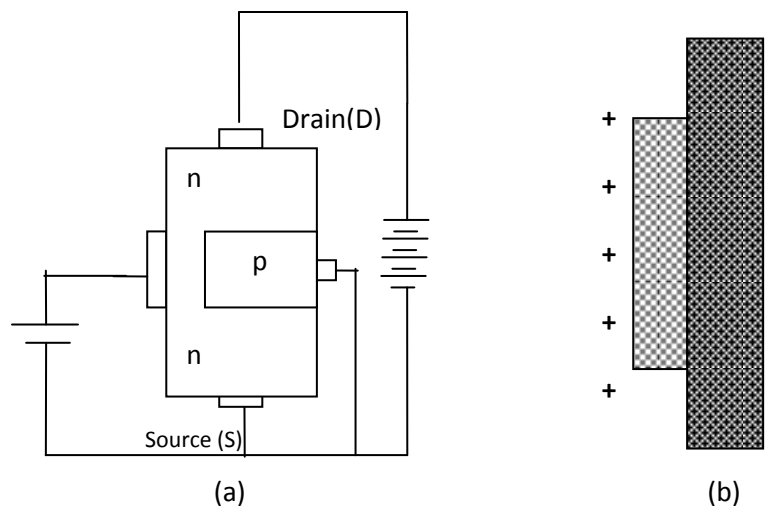


Fig. 4.13



Because these free electrons are added to those already in the channel, the total number of free electrons in the channel is increased. Thus a positive gate voltage enhances or increases the conductivity of the channel. The greater the positive voltage on the gate, greater the conduction from source to drain. Thus by changing the positive voltage on the gate, we can change the conductivity of the channel. Because the action with a positive gate depends upon enhancing the conductivity of the channel, the positive gate operation is called enhancement mode.

The following points are some features about D-MOSFET operation

1. In a D-MOSFET, the source to drain current is controlled by the electric field of capacitor formed at the gate.
2. The gate of a D-MOSFET acts like a capacitor. For this reason it is possible to operate D-MOSFET with positive or negative gate voltage.
3. As the gate of D-MOSFET forms a capacitor, therefore, negligible gate current flows whether positive or negative voltage is applied to the gate. For this reason, the input impedance of D-MOSFET is very high ranging from 10,000 M Ω to 10,000,00 M Ω .
4. The extremely small dimensions of oxide layer under the gate terminal results is a very low capacitance and the D-MOSFET has, therefore, a very low input capacitance. This characteristics makes the D-MOSFET useful in high frequency applications.

E-MOSFET

Figure 4.14 shows the constructional details of n-channel E-MOSFET. Two main features related with E-MOSFET are that it can operate only in enhancement mode and there is no physical channel between source and drain. The minimum gate voltage required to turn E-MOSFET on is called the threshold voltage. Its gate construction is similar to that of D-MOSFET. The substrate extends completely to the SiO₂ layer so that no channel exists. It operates only in the enhancement mode and has no depletion mode. Only by applying VGS of proper magnitude and polarity, the device starts conducting.

 


Fig. 4.14

Symbols used for E-MOSFET

Fig.4.15 (a) shows the schematic symbols for n-channel E-MOSFET and Fig.(4.15 b) shows the schematic symbol for p-channel E-MOSFET.

 


Fig. 4.15

Circuit Operation of E-MOSFET

When $V_{GS} = 0V$, as shown in fig. 4.14(a), there is no channel connecting source and drain. The p-substrate has only a few thermally produced free electrons (minority carriers) so that drain current is almost zero. For this reason, E-MOSFET is normally OFF when $V_{GS} = 0V$.



When V_{GS} is positive, i.e gate is made positive as shown in fig. 4.14(b), it attracts free electrons into the p region. The free electrons combine with the holes next to the SiO_2 layer. If V_{GS} is positive enough, all the holes touching the SiO_2 layer are filled and free electrons begin to flow from the source to drain. The effect is same as creating a thin layer of n-type material i.e. inducing a thin n-layer adjacent to the SiO_2 layer. Thus the E-MOSFET is turned ON and drain current I_D starts flowing from the source to the drain.

When V_{GS} is less than $V_{GS(th)}$, there is no induced channel and the drain current I_D is zero. When V_{GS} is equal to $V_{GS(th)}$, the E-MOSFET is turned ON and the induced channel conducts drain current from the source to the drain. Beyond $V_{GS(th)}$, if the value of V_{GS} is increased, the newly formed channel becomes wider, causing to I_D to increase. If the value of V_{GS} decreases not less than $V_{GS(th)}$, the channel becomes narrower and I_D will decrease.

DEMOSFET-transfer characteristics

The transfer characteristics of D-MOSFET is shown in the fig. 4.16. I_{DSS} is the drain current when $V_{GS}=0V$. As V_{GS} is given negative voltage ($V_{GS}< 0V$), I_D decreases below I_{DSS} and reaches zero when $V_{GS} = (V_{GS})_{off}$. For $V_{GS}>0V$, I_D increases.

The transconductance equation can be written as,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{(V_{GS})_{OFF}} \right)^2$$

The discussion is applicable in principle also to the P-channel DE-MOSFET. For such a device the sign of all currents and voltages in the characteristics must be reversed.

 


FIG. 4.16



Difference between D-MOSFETs and E-MOSFETs:

PARAMETER	D-MOSFETs	E-MOSFETs
Symbols used		
Mode of operation	Depletion and enhancement	Enhancement only
Biasing	<ul style="list-style-type: none"> Gate bias Self bias Zero bias Voltage divider bias 	<ul style="list-style-type: none"> Gate bias Voltage divider bias Drain-feedback bias
Trans conductance curve		



UNIT V : OPERATIONAL AMPLIFIER

Characteristics – slew rate – inverting and non-inverting amplifier – adder – sub tractor – integrator – differentiator

5.1 Operational Amplifiers

Operational amplifiers (Op-amps) have developed from circuits designed for the early analogue computers where they were used for mathematical operations such as addition and subtraction. The design has two inputs and produces an output that is proportional to the difference between the two inputs. Without negative feedback, op amps have an extremely high gain, typically in the hundreds of thousands. Applying negative feedback increases the op amp's bandwidth so they can operate as wideband amplifiers with a bandwidth in the MHz range, but reduces their gain. The operational amplifiers are considered as building blocks of many amplifiers.

An op amp is used to amplify both alternating and direct current signals at the input. The main building blocks or elements of an operational amplifier are two or more differential amplifier stages. This differential stage is followed by a level transistor and output stages. We can construct multistage differential amplifiers for getting desired output gain. For this we can use direct coupling between the successive stages of differential amplifiers.


 


FIG. 5.1

 Block diagram representation of operational amplifiers





In general, the operational amplifiers use a four stage cascaded structure as shown in the fig. 5.2. The four stages of an operational amplifier are as follows,

1. Input amplifier
2. Intermediate amplifier
3. Level shifting stage
4. Output stage

Here the first stage or input amplifier uses a dual input balanced output amplifier. The function of this stage is to provide the high gain for the difference signals. It will also reject the common mode signals enter into the amplifier. Thus, this stage suppresses any undesired noise which is common to both input terminals. The second stage consists of dual input single output differential amplifiers. The function of this stage is also to provide an additional gain to the operational amplifiers. Here there is a direct coupling exists between the first and second stage. This will lead to an output DC level which is well above the ground. Hence in order to reduce this DC level we are using a level shifting stage. This includes an emitter follower element. This stage is also known as a buffer stage. The high input resistance of this stage will help to prevent the loading down the high gain of second stage. The last stage is a push pull amplifier; this will increase the output voltage swing and increases the current supplying capability of operational amplifiers. The resistance of this stage is very low as compared to other stages.

5.2 The characteristics of ideal operational amplifiers are

1. Open loop voltage must be infinite
2. Infinite input resistance
3. Output resistance should remain at zero
4. Bandwidth available must be infinite
5. Perfect balance, this means that the output voltage is zero when the inputs at both terminals are equal.
6. Infinite CMMR value
7. There will be quick change in the output voltage for a small change in the input voltage
8. Stable characteristics against temperature changes



(i) Open loop gain

The main function of an operational amplifier is to amplify the input signal and the more open loop gain it has the better. Open-loop gain is the gain of the op-amp without positive or negative feedback and for such an amplifier the gain will be infinite but typical real values range from about 20,000 to 200,000.

(ii) Input impedance (Z_{in})

Input impedance is the ratio of input voltage to input current and is assumed to be infinite to prevent any current flowing from the source supply into the amplifiers input circuitry ($I_{in} = 0$). Real op-amps have input leakage currents from a few pico-amps to a few milli-amps.

(iii) Output impedance (Z_{out})

The output impedance of the ideal operational amplifier is assumed to be zero acting as a perfect internal voltage source with no internal resistance so that it can supply as much current as necessary to the load. This internal resistance is effectively in series with the load thereby reducing the output voltage available to the load. Real op-amps have output impedances in the 100-20k Ω range.

(iv) Bandwidth (GBW)

An ideal operational amplifier has an infinite frequency response and can amplify any frequency signal from DC to the highest AC frequencies so it is therefore assumed to have an infinite bandwidth. With real op-amps, the bandwidth is limited by the Gain-Bandwidth product (GBW), which is equal to the frequency where the amplifiers gain becomes unity.

(v) Input Offset Voltage (V_{io})

The input offset voltage is a parameter defining the differential DC voltage required between the inputs of an amplifier to make the output zero



5.3 Reason for high popularity of operational amplifiers

- 1) Its characteristics are near to the ideal one
- 2) It is very easy to design
- 3) They work at different levels quite close to the theoretical performance
- 4) It provides high reliability
- 5) It can be available in small packages
- 6) Reduced cost and stable performance against temperature variations

5.4 Operational Amplifier Basics


An op-amp is fundamentally a voltage amplifying device designed to be used with external feedback components such as resistors and capacitors between its output and input terminals. These feedback components determine the resulting function or operation of the amplifier and by virtue of the different feedback configurations whether resistive, capacitive or both, the amplifier can perform a variety of different operations, giving rise to its name of Operational Amplifier.

An *Operational Amplifier* is basically a three-terminal device which consists of two high impedance inputs, one called the Inverting Input, marked with a negative sign, (-) and the other one called the non-inverting Input, marked with a positive or (+).

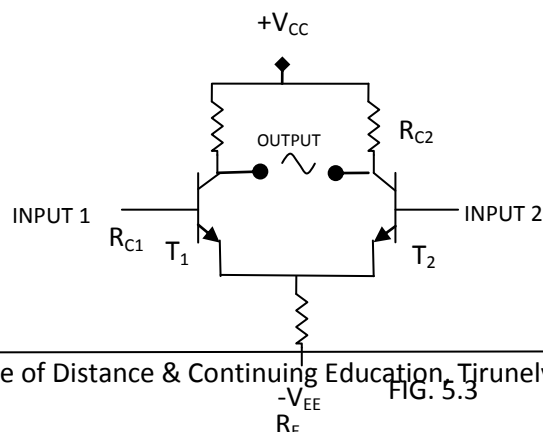5.5 Differential amplifiers

A differential amplifier is a circuit made up of transistors which is used to amplify the difference between the input signals. Here in differential amplifiers, when same input is given to both input terminals then the output voltage will be zero. A small difference in the input voltages may lead to large gain at the output. These types of differential amplifiers has many advantages.

The circuit in fig. 5.3 shows a generalized form of a differential amplifier with two inputs. The two identical transistors T_1 and T_2 are





both biased at the same operating point with their emitters connected together and returned to the common rail, $-V_{EE}$ by way of resistor R_E . The circuit operates from a dual supply $+V_{CC}$ and $-V_{EE}$ which ensures a constant supply. The voltage that appears at the output (V_{out}) of the amplifier is the difference between the two input signals as the two base inputs are in *anti-phase* with each other. So as the forward bias of transistor T_1 is increased, the forward bias of transistor T_2 is reduced and vice versa. Then if the two transistors are perfectly matched, the current flowing through the common emitter resistor, R_E will remain constant.

Operational Amplifiers also have one output of low impedance that is referenced to a common ground terminal and it should ignore any common mode signals, that is, if an identical signal is applied to both the inverting and non-inverting inputs there should no change to the output.

Operational Amplifiers on their own have a very high open loop DC gain and by applying some form of negative feedback, We can produce an operational amplifier circuit that has a very precise gain characteristic that is dependent only on the feedback used.

An op amp only responds to the difference between the voltages on its two input terminals, known commonly as the *Differential Input Voltage* and not to their common potential. Then if the same voltage potential is applied to both terminals the resultant output will be zero. An Operational Amplifiers gain is commonly known as the Open Loop Differential Gain, and is given the symbol (A_0).

5.3 Common Mode Rejection Ratio (CMRR)

CMRR of a differential amplifier measures the ability of the device to reject common-mode signals, that appear simultaneously and in-phase on both amplifier inputs. An ideal differential amplifier would have infinite CMRR; this is not achievable in practice. A high CMRR is required when a differential signal must be amplified in the presence of a possibly large common-mode input. An example is audio transmission over balanced lines. The CMRR is defined as the ratio of the powers of the differential gain over the common-mode gain, measured in positive decibels (using the 20 log rule):



$$CMRR = \frac{A_d}{|A_{cm}|} = 10 \log_{10} \left(\frac{A_d}{A_{cm}} \right)^2 \text{ dB} \quad (5.1)$$

As differential gain should exceed common-mode gain, this will be a positive number, and the higher the better. The CMRR is a very important specification, as it indicates how much of the common-mode signal will appear in the measurement. The value of the CMRR often depends on signal frequency.

It is often important in reducing noise on transmission lines. For example, when measuring the resistance of a thermocouple in a noisy environment, the noise from the environment appears as an offset on both input leads, making it a common-mode voltage signal. The CMRR of the measurement instrument determines the attenuation applied to the offset or noise.

Problem: A differential amplifier has a differential voltage gain of 1V with a differential input of 2.5mV and an output of 2 mV with a common mode input of 5 mV. Find the CMRR in dB.

$$\text{Differential gain } A_{DM} = 1V / 2.5MV = 400$$

$$\text{Common mode gain } A_{CM} = 2MV / 5MV = 0.4$$

$$CMRR_{db} = 20 \log(400/0.4) = 20 \log 1000 = 40 \text{ dB}$$

5.4 Bandwidth of an op amp

Every op amp has its own bandwidth. It depends upon the closed loop gain of the op amp. Gain Band width product (GBW) is defined as

$GBW = A_{CL} \times f = f_{unity}$ where A_{CL} = closed loop gain at the frequency f and f_{unity} is the frequency at which the closed loop gain is unity. The gain-bandwidth product is always constant

An op amp has GBW of 100MHz. Find the band width of the op amp when the closed loop gain value is 100. Find the maximum value of the closed loop gain at 200 KHz.



We know, $GBW = A_{CL} \times f = f_{unity}$ or $f = \frac{GBW}{A_{CL}} = \frac{100MHz}{100} = 1MHz$

Therefore, band width=1MHz

Maximum value of closed loop gain $A_{CL} = \frac{f_{unity}}{f} = \frac{100MHz}{1MHz} = 100$

An opamp has a gain band width product of 1MHz.find the operating band width for the following closed loop gains

- i. $A_{CL}=1$
- ii. $A_{CL}=10$
- iii. $A_{CL}=100$

We know, band width $BW = \frac{GBW}{A_{CL}}$

- i. For $A_{CL}=1$, $BW=1 MHz/1=1MHz$
- ii. For $A_{CL}=10$, $BW=1 MHz/10=100KHz$
- iii. For $A_{CL}=100$, $BW=1MHz/100=10 KHz$

5.5 Slew Rate

The slew rate of an op amp or any amplifier circuit is the rate of change in the output voltage caused by a step change on the input.

It is measured as a voltage change in a given time Its units are $V / \mu s$ or V / ms .

 


FIG. 5.4

A typical general purpose device may have a slew rate of $10 V / \text{microsecond}$. This means that when a large step change is placed on the input, the device would be able to provide an output of 10 volt change in one microsecond. The figures for slew rate change are dependent upon the type of operational amplifier being used. Low power op-amps may only have figures of a volt per microsecond, whereas there are fast operational amplifiers capable to providing rates of $1000 V / \text{microsecond}$.



Op amps may have different slew rates for positive and negative going transitions because of the circuit configuration. They have a complementary output to pull the signal up and down and this means the two sides of the circuit cannot be exactly the same. However it is often assumed that they have reasonably symmetrical performance levels.

5.6 Slewing distortion

If an op amp is operated above its slew rate limit, signals will become distorted. The easiest way to see this is to look at the example of a sine wave. The maximum rate of voltage change occurs at the zero crossing point. Maximum rate of change of sine wave occurs at zero crossing point. It is possible to find the maximum frequency or voltage that can be accommodated. A sine wave with a frequency of f Hertz and peak voltage V volts requires an operational amplifier with a slew rate of $2\pi fV$ volts per second. This is required to ensure the maximum slew rate requirement which occurs at the zero crossing point can be met.

5.7 Op amp slewing distortion limit

Referring to the fig. 5.5, the op amp slewing distortion will result in the creation of a triangular waveform. If the frequency is increased the op amp will be even less able to keep up and therefore the amplitude of the output waveform will decrease. The slew rate may

 


FIG. 5.5

also not be linear over the whole range. As a result the waveform may exhibit a faster rise for the first part of the change, then reverting to the more expected slew rate.

5.8 Slew rate calculation

It is relatively easy to calculate the slew rate of an amplifier that is required for a given application from a knowledge of the maximum voltage and frequency required. To give distortion free operation, for the slew rate of the amplifier, the simple formula below can be used.

$$\text{Slew rate} = 2\pi f v \quad (5.2)$$



where, slew rate is measured in volts / second

f = the highest signal frequency measured in Hz

V = the maximum peak voltage of the signal.

As an example, take the scenario where an op amp is required to amplify a signal with a peak amplitude of 5 volts at a frequency of 25kHz. An op amp with a slew rate of at least $2\pi \times 25\,000 \times 5 = 0.785\text{V}/\mu\text{s}$ would be required.

5.9 Frequency response of an op amp:

- [1] Maximum operating frequency = $\frac{\text{slew rate}}{2\pi V_{pk}}$
- [2] Peak output voltage limits the maximum operating frequency
- [3] When the frequency exceeds the maximum value, output will get distorted
- [4] If the operating frequency exceeds a certain value then, decrease in input impedance, increase in output impedance, decrease in open loop voltage gain will result

5.10 Virtual ground

In electronics, a virtual ground is a node of a circuit that is maintained at a steady reference potential, without being connected directly to the reference potential. The node is called ground or earth. A voltage divider, using two resistors, can be

 


Fig. 5.6

used to create a virtual ground node. If two voltage sources are connected in series with two resistors, it can be shown that the midpoint becomes a virtual ground. Since an operational amplifier has very high open-loop gain, the potential difference between its inputs tend to zero when a feedback network is implemented. To achieve a reasonable voltage at the output, the output supplies the inverting input through the feedback network with enough voltage to reduce the potential difference between the inputs to microvolts. The non-inverting (+) input of the operational amplifier is grounded. Therefore, its inverting



(-) input, although not connected to ground, will assume a similar potential, becoming a virtual ground if the op amp is working in its linear region.

5.11 Inverting amplifier

Inverting amplifier is one in which the output is exactly 180° out of phase with respect to input. That is the output is an inverted amplified version of the input. Circuit operation The inverting amplifier using op amp is shown in the fig. 5.7

Assuming the op amp is an ideal and applying the concept of virtual short at the input terminals, the voltage at the inverting terminal is equal to non inverting terminal. Applying Kirchoff's Current Law at the inverting node,

$$\frac{0 - V_i}{R_i} + \frac{0 - V_o}{R_f} = 0$$

By rearranging the terms we will get

$$\text{Voltage gain } A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

 


FIG. 5.7

Hence, Gain of inverting amplifier $A_v = -\frac{R_f}{R_i}$

Features of inverting amplifiers

1. Closed loop voltage gain is independent of internal open loop voltage gain. Thus negative feedback stabilises the voltage gain.
2. If $R_f = R_i$, voltage gain = -1. Thus the circuit provides unity voltage gain with 180° phase inversion.
3. If R_f is some multiples of R_i then the voltage gain is constant. If precise values are selected for R_f and R_i we get a wide range of voltage gains. Thus by fixing the values for R_f and R_i , inverting amplifier provides constant voltage gain.



5.12 Non-inverting amplifier

Non Inverting amplifier is one in which the output is in phase with respect to input. That is if we apply a positive voltage at the input, output will be positive. Output is a Non inverted amplified version of input. A non-inverting amplifier is designed by using op amp as shown in the fig.5.8. The input signal is applied to the non inverting input (+). The output is feedback to the input through the

 


FIG. 5.8

voltage divider arrangement formed by R_f and R_i . This provides negative feedback. Signal is applied to non inverting input and the output is non inverted.

Gain of the amp.

Since the input impedance of op amp is very high, all current that flows through R_f will flow through R_i . From the circuit,

$$\text{Voltage across } R_i = V_{in} - 0$$

$$\text{Voltage across } R_f = V_{out} - V_{in}$$

Current through R_i = current through R_f

$$\text{ie. } \frac{(V_{in} - 0)}{R_i} = \frac{(V_{out} - V_{in})}{R_f}$$

$$\frac{V_{out}}{V_{in}} = \frac{(R_f + R_i)}{R_i} = 1 + \frac{R_f}{R_i}$$

This gives the closed loop voltage gain of non inverting amplifier.

5.15 Features of non inverting amplifier

1. Voltage gain depends on the values of R_f and R_i
2. Voltage gain is greater than or equal to 1



3. Voltage gain is positive

5.13 Voltage Follower

The voltage follower shown in Fig. 5.9 is like a non inverting voltage amplifier, but without its feedback and input resistors. The gain of a non inverting voltage amplifier would normally be described using the values of R_f and R_{in} by the formula:

$$A_{vcl} = 1 + \frac{R_f}{R_i}$$

 


FIG. 5.9

In the voltage follower circuit however, both R_i and R_f are replaced by simple conductors, and so both these values in the above formula will be extremely small, therefore the gain is 1. The voltage follower does not therefore, act as an amplifier, the output voltage follows the input voltage, but the circuit does have some very useful properties

5.14 (i) Summing amplifier

An op amp can be used for summing two or more voltages the voltage sources V_1 , V_2 , and V_3 are connected to the inverting input terminals through the resistors R_1 , R_2 and R_3 . The non-inverting terminal is grounded. The output is fed back to the inverting input through a feedback resistor R_f ,

According to kirchoff's law the current entering into S is equal to the current leaving S

$$ie. \quad I_1 + I_2 + I_3 = I$$

since the summing point is at zero potential, we can write

 


Fig. 5.10

$$\frac{(V_1 - 0)}{R_1} + \frac{(V_2 - 0)}{R_2} + \frac{(V_3 - 0)}{R_3} = \frac{(0 - V_0)}{R_f}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_0}{R_f} \quad (5.4)$$

$$\text{or } V_0 = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

If we consider $R_1 = R_2 = R_3 = R_f$ then, $V_0 = -(V_1 + V_2 + V_3)$

Thus we get the output as the inverted sum of the inputs.

(ii) Subtracting amplifier

The subtracting amplifier is otherwise called difference amplifier. The circuit (Fig. 5.11) is just a combination of an inverting and non inverting amplifier. We will find the output voltages of these two configurations separately and then summing them will give the overall output voltage. From the circuit given, If V_b is made zero, the circuit becomes an inverting amplifier. The output voltage V_{oa} due to V_a alone can be expressed using the following equation.

$$V_{oa} = -\frac{R_f}{R_1} V_a \quad (5.5)$$

When V_a is made zero the circuit becomes a non inverting amplifier. Let V_1 be the voltage at the non inverting input pin. Relation between V_b and V_1 can be expressed using the following equation.



$$V_1 = \frac{V_b}{R_2 + R_3} R_3 \quad (5.6)$$

Output voltage V_{ob} due to V_b alone is according to the equation

 


Fig. 5.11

$$V_{ob} = \frac{V_b}{R_2 + R_3} R_3 \left(1 + \frac{R_f}{R_1} \right) \quad (5.7)$$

Let $R_1 = R_2$ and $R_3 = R_f$, then

$$\begin{aligned} V_{ob} &= \frac{V_b}{R_1 + R_f} R_f \left(1 + \frac{R_f}{R_1} \right) \\ &= \left(\frac{R_f}{R_1 + R_f} \right) \left(\frac{R_1 + R_f}{R_1} \right) V_b \\ &= \left(\frac{R_f}{R_1} \right) V_b \end{aligned} \quad (5.8)$$

Then overall output voltage is

$$\begin{aligned} V_0 &= V_{oa} + V_{ob} \\ &= -\frac{R_f}{R_1} V_a + \frac{R_f}{R_1} V_b \\ &= -\frac{R_f}{R_1} (V_a - V_b) \end{aligned}$$



If we choose $R_f = R_1$, Then $V_0 = -(V_a - V_b)$ (5.9)

If an op. amp. is connected with a feedback resistor $R_f = 10000$ ohms and the signal is connected to the inverting input terminal through a resistance of $R = 1000$ ohms with non-inverting input terminal grounded, what is the gain of the amplifier?

We know, voltage gain of the amplifier $A = -R_f/R = -10^4/10^3 = -10$

So gain = - 10

Three voltage sources of e.m.f. 1V, 2V and 3V are connected through the resistors 1 Mega ohms, 2 Mega ohms, 5 Mega ohms respectively. If the feedback resistance is 10 Mega ohms, find the output voltage.

Output voltage of an adder is given by

$$\begin{aligned}
 V &= -\left[\left(\frac{R_f}{R_1}\right)V_1 + \left(\frac{R_f}{R_2}\right)V_2 + \left(\frac{R_f}{R_3}\right)V_3\right] \\
 &= -\left[\frac{10 \times 10^6}{1 \times 10^6} + \frac{10 \times 10^6}{2 \times 10^6} + \frac{10 \times 10^6}{5 \times 10^6}\right] \\
 &= -[10 + 5 + 2] = -17 \text{ volts}
 \end{aligned}$$

5.17 (I) OP-AMP DIFFERENTIATOR

The circuit which produces the differentiation of the input voltage at its output is called differentiator. The following circuit diagram shows the differentiator using op-am. Assume

 


Fig. 5.12



current I is flowing through capacitor C . It is given as

$$I = C \frac{d}{dt}(V_{in} - 0)$$
$$= C \frac{dV_{in}}{dt}$$

Since input current to the op-amp is zero, same current ' I ' flows through resistance R as shown. It is given by

$$I = \frac{(0 - V_0)}{R}$$


Equating both the above equations of ' I ' we get,

$$-\frac{V_0}{R} = C \frac{dV_{in}}{dt}$$
$$\text{or } V_0 = -RC \frac{dV_{in}}{dt}$$

Thus output voltage is nothing but time differentiation of the input signal and hence acting as differentiator. Here RC is the time constant of the differentiator.

Integrator

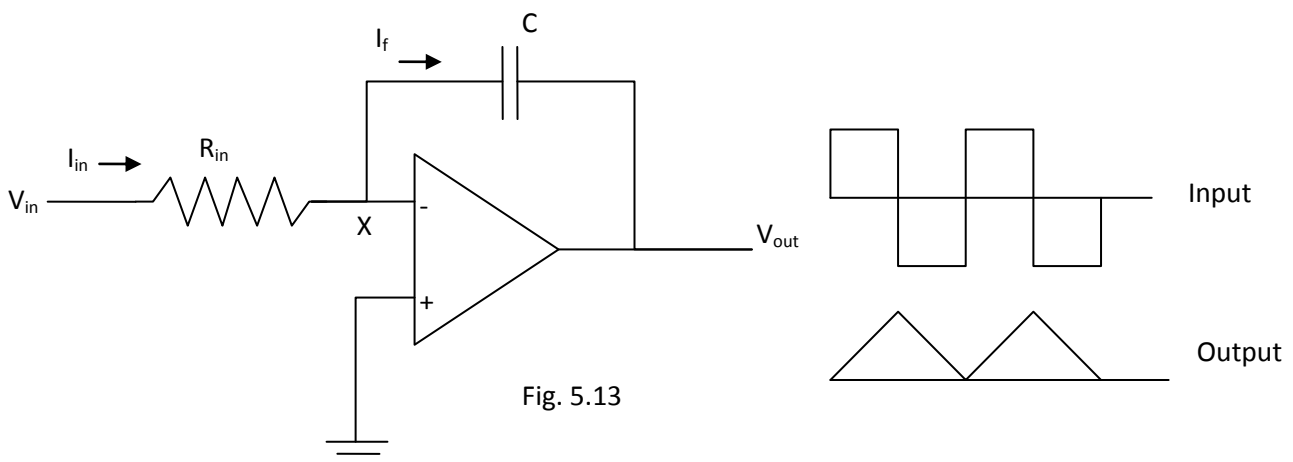The integrator circuit using op amp is shown in the fig. 5.13. The voltage across the capacitor is output $-V_{out} = Q/C$, where Q is the charge stored on the capacitor. If the capacitor is charging and discharging, the rate of change of voltage across the capacitor is given by,





$$V_C = \frac{Q}{C}$$
$$V_C = V_X - V_{out} = 0 - V_{out}$$
$$\therefore -\frac{dV_{out}}{dt} = \frac{dQ}{Cdt} = \frac{1}{C} \frac{dQ}{dt}$$

But dQ/dt is electric current and since the node voltage of the integrating op-amp at its inverting input terminal is zero, $X = 0$, the input current I_{in} flowing through the input resistor R_{in} is given as:

$$I_{in} = \frac{V_{in} - 0}{R_{in}} = \frac{V_{in}}{R_{in}}$$

The current flowing through the feedback capacitor C is given as:

$$I_f = C \frac{dV_{out}}{dt} = C \frac{dQ}{Cdt} = \frac{dQ}{dt}$$

Assuming that the input impedance of the op-amp is infinite (ideal op-amp), no current flows into the op-amp terminal. Therefore, the nodal equation at the inverting input terminal is given as:

$$I_{in} = I_f = \frac{V_{in}}{R_{in}} = C \frac{dV_{out}}{dt}$$

$$\text{Or } \frac{dV_{out}}{dt} = \frac{1}{C R_{in}} V_{in}$$

$$\text{Or } V_{out} = \frac{1}{CR_{in}} \int V_{in} dt$$

Thus the output voltage is the integral value of the input voltage.

Prepared by
Dr. V. RAVICHANDRAN
Department of Physics
Sri K.G.S Arts College, Srivaikuntam.